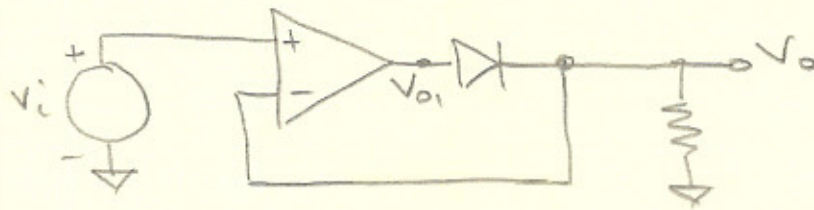


Precision Rectification "Super Diode"





$V_i > 0 \Rightarrow$ neg feedback $\Rightarrow V_{o1} = 0$


$V_i < 0 \Rightarrow$ no neg feedback \Rightarrow

$$\begin{aligned} V_{ID} &= +V_i \\ V_{o1} &= -V_{cc} \\ V_o &= 0 \end{aligned}$$

Limiter Circuit

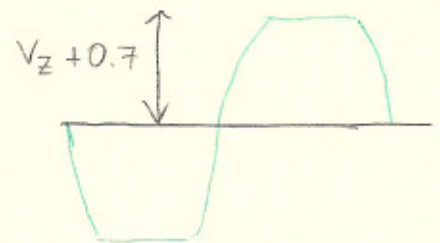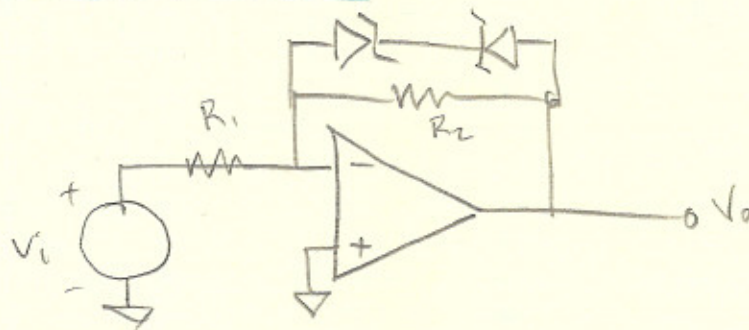

Logarithmic Amplifier

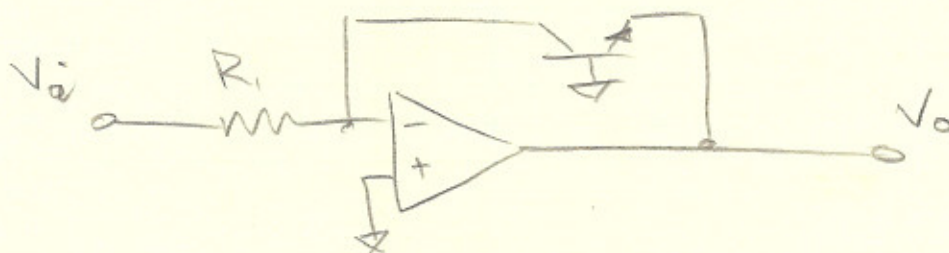


$V_I > 0$ & $V_O < 0$ } then we have negative feedback.

$$i_1 = \frac{V_I}{R_1} = I_S \exp\left(-\frac{V_O}{V_T}\right)$$


$$\frac{V_I}{R_1 I_S} = \exp\left(-\frac{V_O}{V_T}\right)$$

$$\therefore V_O = -V_T \ln\left(\frac{V_I}{R_1 I_S}\right)$$

Note exponential amplifier

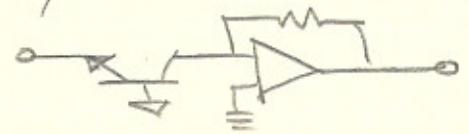

Integrator


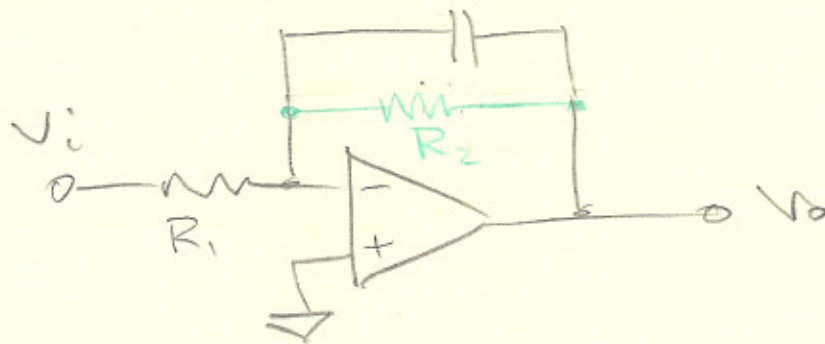


$$i_1 = \frac{V}{R_1} = C \frac{dV_C}{dt} = -C \frac{dV_O}{dt}$$

$$\frac{dV_O}{dt} = -\frac{1}{R_1 C} V_I$$

$$V_O = -\frac{1}{R_1 C} \int_0^t V_I dt$$

Now adding R_2 b/c of offset voltage.

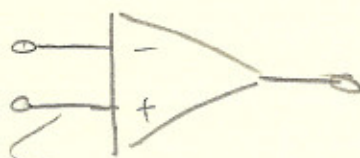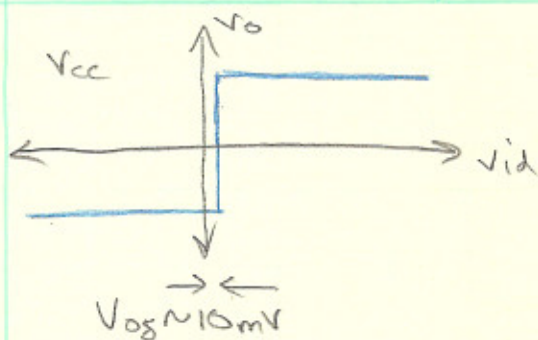


there really should be a supply equal to V_{os} in our theoritical op amp.

$$i_1 = -\frac{V_{os}}{R_1} = C \frac{dV_c}{dt} = C \frac{d(V_{os} - V_o)}{dt} = \underbrace{C \frac{dV_{os}}{dt}}_{\text{assume zero}} - C \frac{dV_o}{dt}$$

$$V_o = + \frac{1}{RC} \int_0^t V_{os} dt + V_o(0)$$

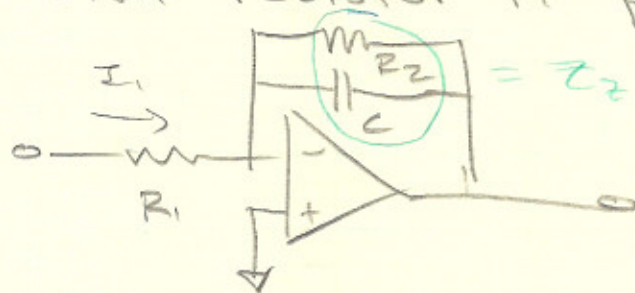here we see that the voltage grows forever because of the offset voltage.
But with resistor in place.



$$Z_2 = [R_2^{-1} + j\omega C]^{-1}$$

$$I_1 = \frac{V_s}{R_1} = \frac{-V_o}{Z_2} = -V_o \left(\frac{1}{R_2} + j\omega C \right)$$

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega C}$$