

H/w:

FIND THE INVERSE OF:

① $F(s) = \frac{s}{(s+1)(s+2)^2}$

ans for ①

$$f(t) = \left\{ -e^{-t} + e^{-2t} + 2te^{-2t} \right\}$$


②

$$F(s) = \frac{16}{s^2(s+4)}$$

ans for ②

$$f(t) = \left\{ 4t - te^{-4t} \right\} u(t)$$

TWO PORT NETWORKS

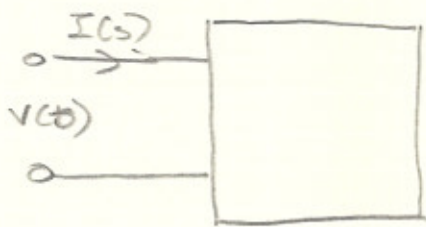


$$\frac{V(s)}{I(s)} = Z(s)$$

$$\frac{I(s)}{V(s)} = Y(s)$$

this is known as a one port network.

a practical example.

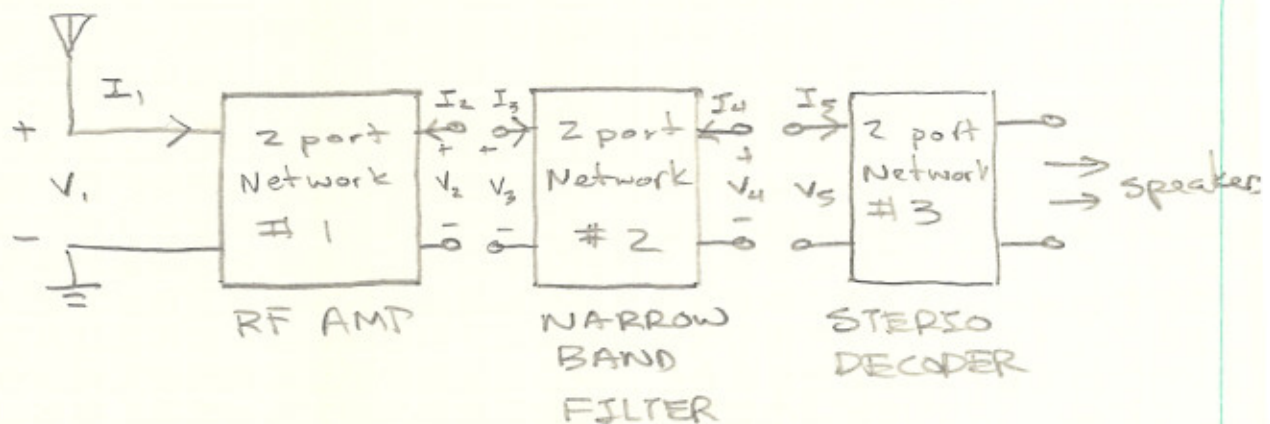

modular Receiver design by interconnected 2 ports.

ANALYSIS OF 2 PORT NETWORKS


1. OPEN CIRCUIT IMPEDANCE PARAMETERS OR Z PARAMETERS.

a set of equations that completely describe the 2 port, z-parameters network may be written as.

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

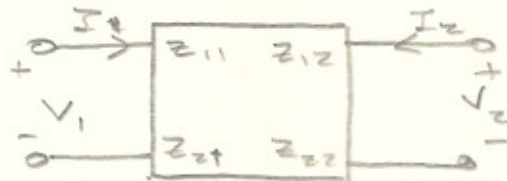it is assumed that all values are Laplace Transform quantities.



when $I_2 = 0$, then

$$\left. \frac{V_1(s)}{I_1(s)} \right|_{I_2=0} = Z_{11} \quad (\text{in port driving point impedance})$$

$$\left. \frac{V_2(s)}{I_1(s)} \right|_{I_2=0} = Z_{21} \quad (\text{open circuit transfer impedance})$$

when $I_1 = 0$


$$\left. \frac{V_1(s)}{I_2(s)} \right|_{I_1=0} = Z_{12} \quad (\text{open circuit transfer impedance})$$

$$\left. \frac{V_2(s)}{I_2(s)} \right|_{I_1=0} = Z_{22} \quad (\text{output driving pt impedance looking into port 2})$$

From Above

$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \underbrace{\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}}_{\text{impedance matrix}} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

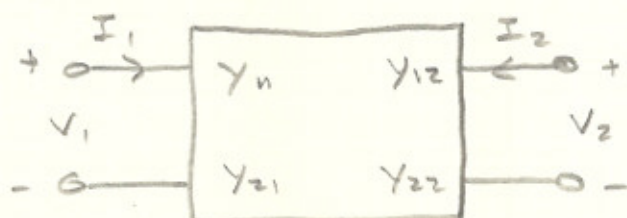2. SHORT CIRCUIT ADMITANCE PARAMETERS OR Y-PARAMETERS



$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_{11}$$

(driving pt admittance)

$$\left. \frac{I_2}{V_1} \right|_{V_2=0} = Y_{21}$$

transfer admittance

$$\left. \frac{I_1}{V_2} \right|_{V_1=0} = Y_{12}$$

transfer admittance


$$\left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_{22}$$

driving pt admittance

and we have

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

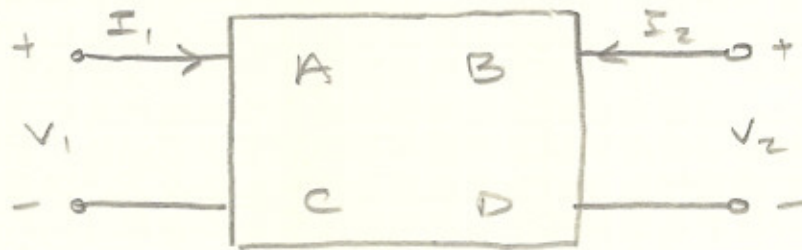3. CHAIN OR ABCD MATRIX (TRANSFER PARAMETERS)



equations are

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

in matrix form,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

EX:

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\frac{V_1}{Z_{11}} = I_1 + \frac{Z_{12}I_2}{Z_{11}}$$

$$\frac{V_2}{Z_{21}} = I_1 + \frac{Z_{22}I_2}{Z_{21}}$$

$$\frac{V_1}{Z_{11}} - \frac{V_2}{Z_{21}} = \left(\frac{Z_{12}}{Z_{11}} - \frac{Z_{22}}{Z_{21}} \right) I_2$$

$$\frac{V_1}{Z_{11}} = \frac{V_2}{Z_{21}} + \left(\frac{Z_{12}Z_{21} - Z_{11}Z_{22}}{Z_{11}Z_{21}} \right) I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{|Z|}{Z_{21}} I_2$$

$$\therefore A = \frac{Z_{11}}{Z_{21}} \quad B = \frac{|Z|}{Z_{21}}$$

and now solving for C & D.

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 - Z_{22} I_2 = Z_{21} I_1$$

$$I_1 = \frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2$$

$$C = \frac{1}{Z_{21}} \quad D = \frac{Z_{22}}{Z_{21}}$$


Z PARAMETERS & Y-PARAMETERS

$$\underline{Y} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \underline{Z}^{-1}$$


$$\underline{Y} = \frac{1}{|\underline{Z}|} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$

note: adjoint method.

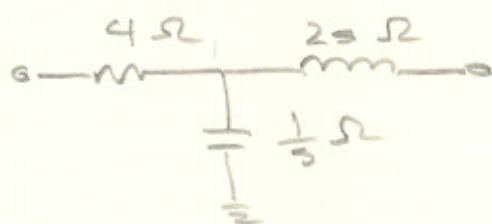EX: determine the z-parameters for the domain network.




SOL:

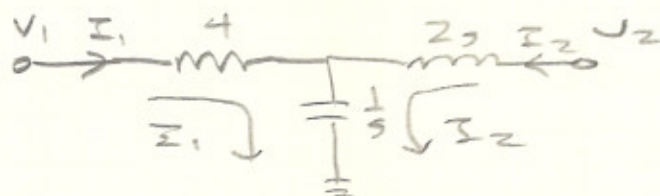

$$V_1 = (4 + \frac{1}{3}) I_1 - (\frac{1}{3}) I_2$$

$$V_2 = (-\frac{1}{3}) I_1 + (2 + \frac{1}{3}) I_2$$

EX: find the z parameters of

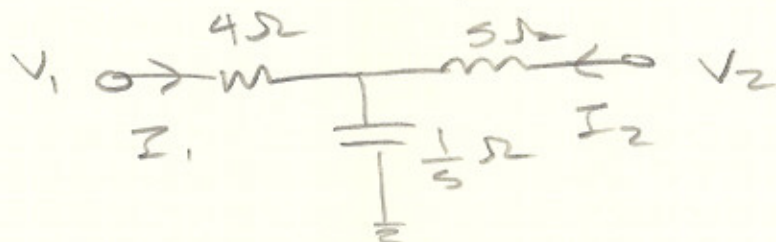

SOL:

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{4s+1}{s}$$

$$z_{21} = \frac{1}{s} = z_{12}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{2s^2+1}{s}$$

$$\therefore Z(s) = \begin{bmatrix} \frac{4s+1}{s} & \frac{1}{s} \\ \frac{1}{s} & \frac{2s^2+1}{s} \end{bmatrix}$$

EX: for the same circuit find the y parameters.

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

SOL:

$$\left. \frac{I_1}{V_1} \right|_{V_2=0} = y_{11} = \frac{2s^2+1}{8s^2+2s+4}$$

$$\frac{I_1}{I_2} \Big|_{V_2=0} = -D$$

$$V_x = -2sI_2$$

$$I_1 + I_2 = (V_x)s$$

divide by I_2 , sub for V_x , we get

$$\frac{I_1}{I_2} + 1 = -2s^2$$

$$\therefore -D = -2s^2 - 1 \quad \therefore D = 2s^2 + 1$$

$$\frac{V_1 - V_x}{4} = I_1, \quad V_x = -2sI_2$$

and

$$I_1 = sV_x - I_2 \quad \text{from } I_1 + I_2 = sV_x$$

$$\therefore I_1 = -(2s^2 + 1)I_2$$

$$\frac{V_1 + 2sI_2}{4} = -(2s^2 + 1)I_2$$

$$V_1 + 2sI_2 = -4(2s^2 + 1)I_2$$

$$\left. \frac{V_1}{I_2} \right|_{V_2=0} = -4(2s^2+1) - 2s = -8$$

$$\therefore B = 8s^2 + 2s + 1$$

$$\underline{T}(s) = \begin{bmatrix} 4s+1 & 8s^2+2s+1 \\ s & 2s^2+1 \end{bmatrix}$$

HYBRID PARAMETERS (h-parameters)
AND G PARAMETERS.

$$G = H^{-1}$$

the h-parameters are useful in the analysis of electronic circuits, containing transistors etc... These parameters are a mixed set.

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

in matrix form

$$\underline{H} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$$

The values of the individual h parameters can be determined from measurement or from calculations under short and open circuit conditions.

$$h_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0} = \text{---} \Omega$$


$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0} = \text{---} \text{ (voltage gain)}$$

$$h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0} = \text{---} \text{ (current gain)}$$

$$h_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0} = \text{---} \text{ } \frac{1}{\Omega}$$


Unit of Siemens for admittance

EX: given

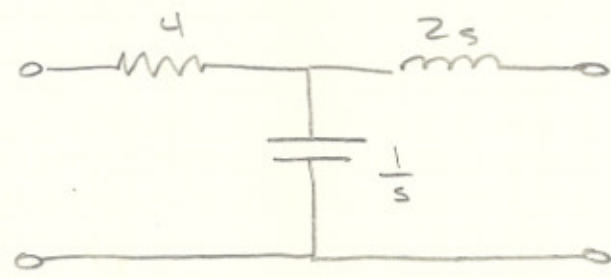


find the H-parameters.

SOL: Circuit A. $V_2=0$

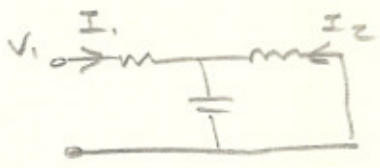

Circuit B. $I_1=0$

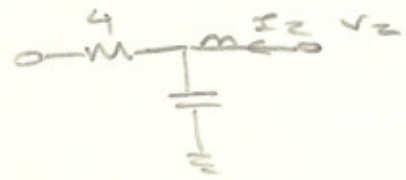

from circuit (a) with $V_2(s) = 0$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = 4 + \frac{2s\left(\frac{1}{s}\right)}{2s + \left(\frac{1}{s}\right)}$$
$$= \frac{8s^2 + 2s + 4}{2s^2 + 1}$$

the value of $I_2(s)$ can be obtained from current divider

$$I_2(s) = \frac{\left(-\frac{1}{s}\right) I_1}{2s + \left(\frac{1}{s}\right)}$$

$$I_2(s) = \frac{-1}{2s^2 + 1} I_1(s)$$

$$\therefore h_{21} = \frac{-1}{2s^2 + 1}$$

The other Z parameters are determined from open circuit condition with $I_1 = 0$ as shown in figure (B), so that


$$V_1 = \left(\frac{\frac{1}{s}}{2s + \frac{1}{s}} \right) V_2(s)$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{1}{2s^2 + 1}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{s}{2s^2 + 1}$$

$$\underline{H}(s) = \begin{bmatrix} \frac{3s^2 + 2s + 4}{2s^2 + 1} & \frac{1}{2s^2 + 1} \\ \frac{-1}{2s^2 + 1} & \frac{5}{2s^2 + 1} \end{bmatrix}$$


H/w: determine h parameters.

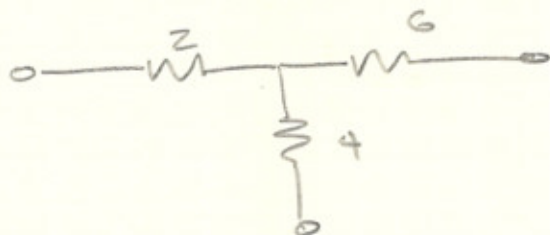

SOL:

$$\underline{H} = \begin{bmatrix} \frac{22}{5} & \frac{2}{5} \\ -\frac{2}{5} & \frac{1}{10} \end{bmatrix}$$

Ex: find the y -parameters of

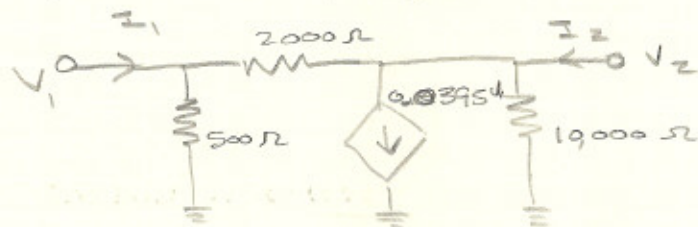


SOL

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$\left. \frac{I_1}{V_1} \right|_{V_2=0} = y_{11}$$

$$\left. \frac{I_2}{V_1} \right|_{V_2=0} = y_{21}$$

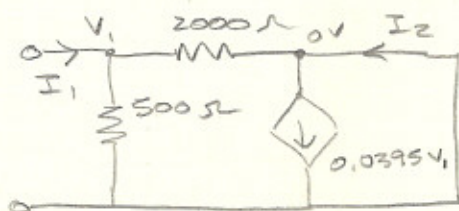


10 k Ω resistor is gone
b/c it is shorted out.

$$I_1 \Big|_{V_2=0} = \frac{V_1}{500} + \frac{V_1}{2000}$$

$$\frac{I_1}{V_1} = \frac{2000 + 500}{(2000)(500)} = y_{11} = 2.5 \text{ mS}$$

$$I_2 = \frac{0.0395 V_1}{\frac{V_1}{2000}} = 39 \text{ mS}$$

for y_{12} and y_{22} , when $V_1 = 0$

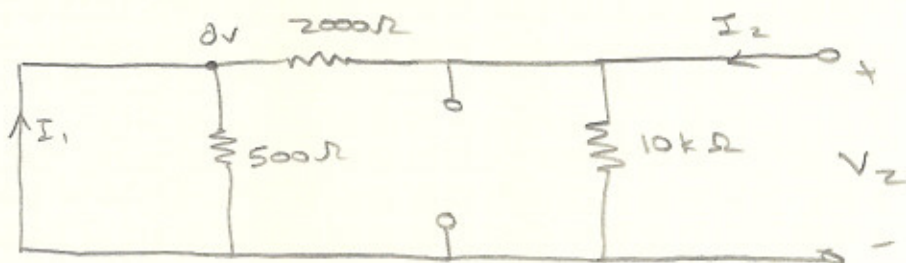

$$I_2 = \frac{V_2}{10,000} + \frac{V_2}{2000}$$


$$\left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_{22} = 0.6 \text{ mS}$$

$$I_1 = -\frac{V_2}{2000}$$

$$\left. \frac{I_1}{V_2} \right|_{V_1=0} = Y_{12} = -0.5 \text{ mS}$$

$$\underline{Y} = \begin{bmatrix} 2.5 & -0.5 \\ 39 & 0.6 \end{bmatrix} \quad \text{where } \text{S} = \text{mho} = \Omega^{-1}$$


Ex: find the h-parameters given for.

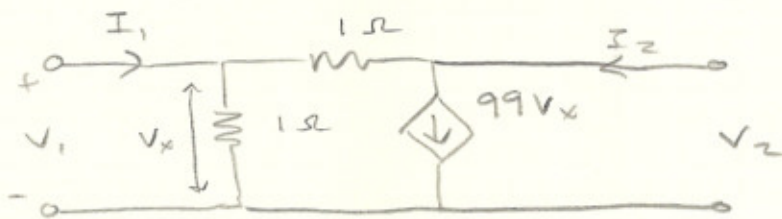

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

SOL: make $V_2 = 0$

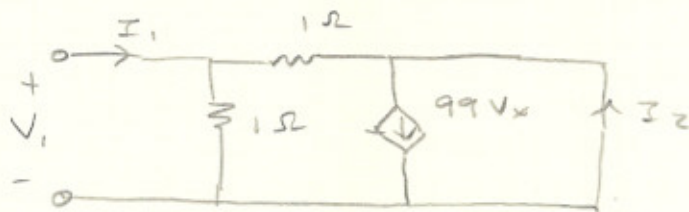

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$


$$I_1 = \frac{V_1}{1} + \frac{V_1}{1} = 2V_1$$

$$\therefore h_{11} = \frac{1}{2} = 0.5 \Omega$$

$$I_2 = \frac{V_1}{1} - 99V_1 = -98V_1$$

$$\therefore h_{21} = 49$$

for h_{12} & h_{22} , $I_1 = 0$

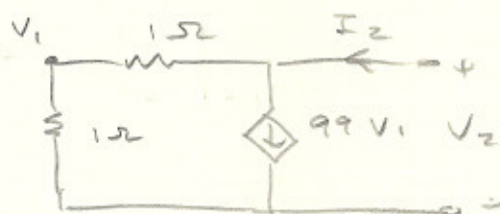


$$I_2 = 99V_1 + \frac{99V_1 - V_1}{1}$$

$$= 197$$

did not finish

ans $\begin{bmatrix} 0.5 & 0.5 \\ 49 & 50 \end{bmatrix}$

THE SERIES CONNECTION.

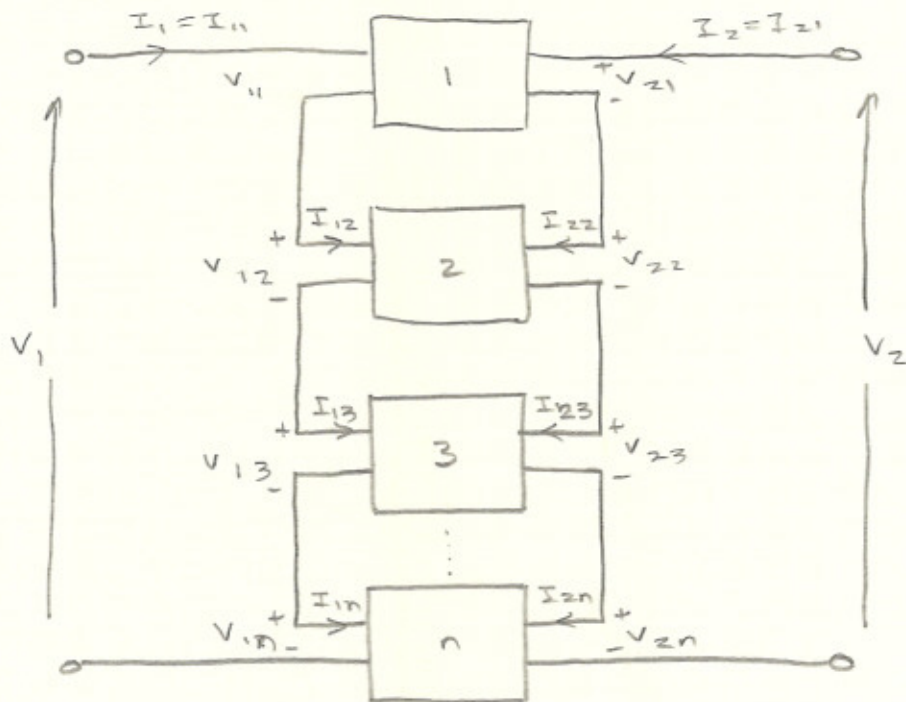

KVL applies, and in matrix form

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_{11} \\ V_{21} \end{bmatrix} + \begin{bmatrix} V_{12} \\ V_{22} \end{bmatrix} + \begin{bmatrix} V_{13} \\ V_{23} \end{bmatrix} + \dots + \begin{bmatrix} V_{1n} \\ V_{2n} \end{bmatrix}$$

as seen

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{11} \\ I_{21} \end{bmatrix} = \begin{bmatrix} I_{12} \\ I_{22} \end{bmatrix} = \begin{bmatrix} I_{13} \\ I_{23} \end{bmatrix} = \begin{bmatrix} I_{1n} \\ I_{2n} \end{bmatrix}$$




each \underline{V} is related to its own current vector \underline{I} by the \underline{z} parameters (ie- $\underline{V} = \underline{z}\underline{I}$) then

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underline{z}_1 \begin{bmatrix} I_{11} \\ I_{21} \end{bmatrix} + \underline{z}_2 \begin{bmatrix} I_{12} \\ I_{22} \end{bmatrix} + \underline{z}_3 \begin{bmatrix} I_{13} \\ I_{23} \end{bmatrix} + \dots + \underline{z}_n \begin{bmatrix} I_{1n} \\ I_{2n} \end{bmatrix}$$

since the vectors are equal, then.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \left\{ \underline{z}_1 + \underline{z}_2 + \underline{z}_3 + \dots + \underline{z}_n \right\} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underline{z}_{eq} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

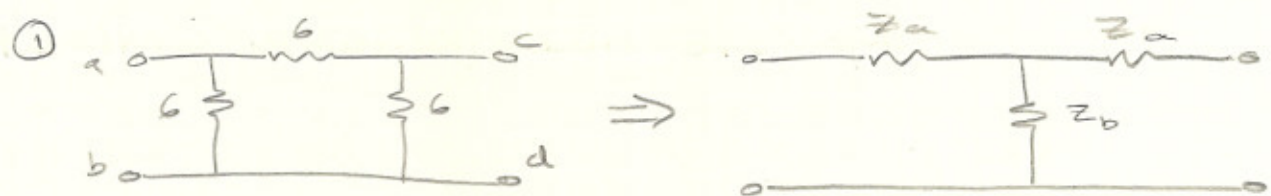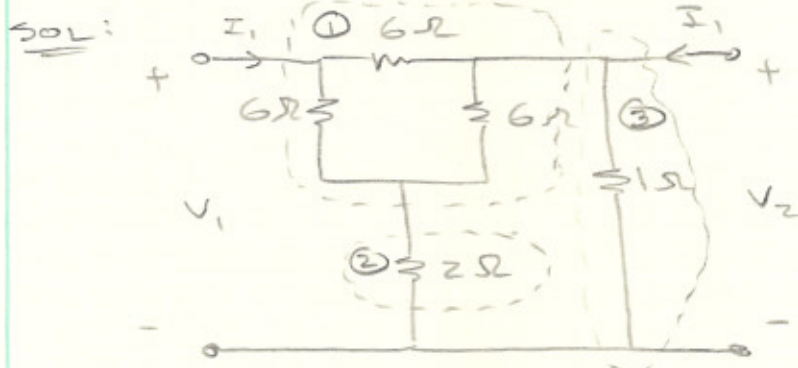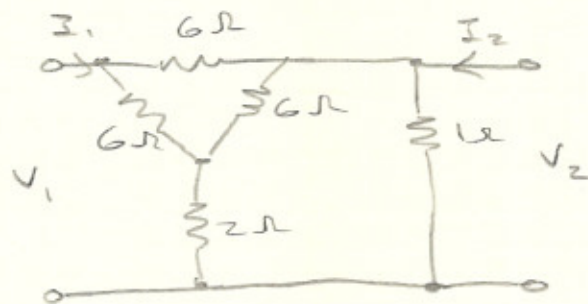Ex: reduce the circuit shown to equivalent Pi network.



$$Z_{ab} = 6 // (6 + 6) = 4 \Omega$$

$$Z_{cd} = 6 // (6 + 6) = 4 \Omega$$

so $Z_{11} = Z_{ab} = 4 \Omega$

$$Z_{22} = Z_{cd} = 4 \Omega$$

but $Z_{11} \neq Z_{ab} = Z_a + Z_b = 4 \Omega$

$$Z_{22} = Z_{cd} = Z_a + Z_b = 4 \Omega$$

$$\therefore Z_b = 2 \Omega$$

Then we convert Pi network ① to a balanced Tee network, the tee elements will be $1/3$ those of the Pi network.

$$\therefore \underline{Z} = \begin{bmatrix} z+2 & z \\ z & z+2 \end{bmatrix}$$

the single shunt element of ② has the T representation of

$$\underline{T}_2 = \begin{bmatrix} 1 & 0 \\ \frac{1}{2} & 0 \end{bmatrix} \xRightarrow{\text{table}} \begin{bmatrix} z & z \\ z & z \end{bmatrix} = \underline{Z}_{eq}(z)$$

although the matrix is singular, it may still be used to form an equivalent \underline{Z}_{eq} for the series

combinations of the subnetworks ① & ②

$$\underline{Z}_{eq}(1+2) = \underline{Z}_1 + \underline{Z}_2 = \begin{bmatrix} 6 & 4 \\ 4 & 6 \end{bmatrix}$$

\underline{Z}_{eq} is not singular, $\Delta \underline{Z}_{eq} = 20$, from the Table, we convert \underline{Z}_{eq} to \underline{T}_{12}

$$\underline{T}_{12} = \begin{bmatrix} \frac{3}{2} & 5 \\ \frac{1}{4} & \frac{3}{2} \end{bmatrix}$$

Combinations of ① & ② are in cascade with ③

$$\underline{T}_3 = \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$

\therefore

$$\underline{T}_{eq} = \underline{T}_{12} \underline{T}_3 = \begin{bmatrix} \frac{13}{2} & 5 \\ \frac{7}{4} & \frac{3}{2} \end{bmatrix}$$

$$\Delta T_{eq} = 1$$

from table, we convert \underline{Y}_{eq} to \underline{Y}_{eq} to obtain Pi network

$$\underline{Y}_{eq} = \begin{bmatrix} \frac{3}{10} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{13}{10} \end{bmatrix}$$

