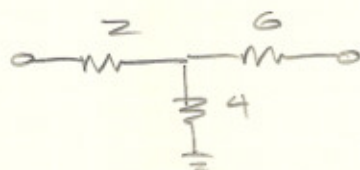


here we notice that $g_{12} = -g_{21}$

H/w:



ans:

$$\underline{G} = \begin{bmatrix} \frac{1}{6} & -\frac{2}{3} \\ \frac{2}{3} & \frac{22}{3} \end{bmatrix}$$

note: also prove that $\underline{G}^{-1} = \underline{H}$

INTERCONNECTION OF 2 PORT NETWORK


the power and versatility of a simple one port network is not obvious because of their limited behaviour as individual one ports.

from RC pairs emerged low pass, high pass and band pass / band stop filters.

Interconnections of operational amplifiers gave building blocks which yielded circuits of very high gain, which are extensively used in practical circuits.

THE CASCADE CONNECTION

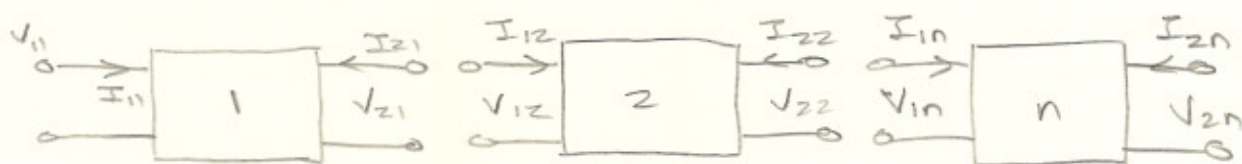consider the n 2-port networks connected in cascade. the configuration can be reduced to one that can be represented by equivalent transmission parameter matrix " T ".



Consider the 2 ports 1 and 2, and write

$$\begin{bmatrix} V_{11} \\ I_{11} \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_{21} \\ -I_{21} \end{bmatrix}$$

$$\begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_{22} \\ -I_{22} \end{bmatrix}$$

At the junction of 2 ports 1 and 2, voltages must match and KCL

$$I_{12} = -I_{21},$$

then we may write

$$\begin{bmatrix} V_{21} \\ -I_{21} \end{bmatrix} = \begin{bmatrix} V_{12} \\ I_{12} \end{bmatrix}$$

henceforth


$$\begin{bmatrix} V_{11} \\ I_{11} \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_{22} \\ -I_{22} \end{bmatrix}$$

then we can find the equivalent circuit.


$$\begin{bmatrix} A_{eq} & B_{eq} \\ C_{eq} & D_{eq} \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

Cascade algorithm is very useful where ladder networks required reduction to a simple equivalent such as Tee or Pi networks or a simple admittance or impedance

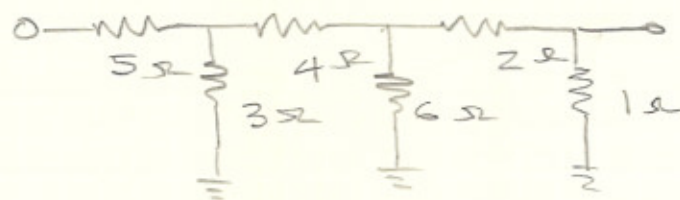
EX: consider the following ladder network consisting of 6 resistors. Reduce it to a single Tee equivalent.



SOL (method I):

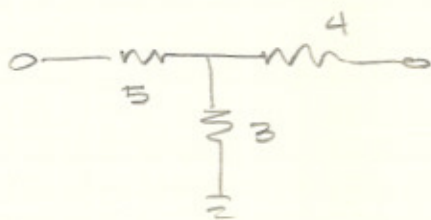

sub net 1

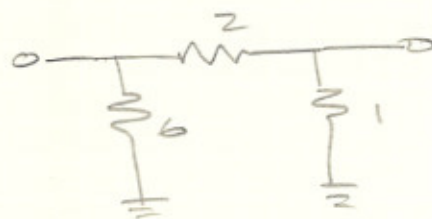

sub net 2

$$\underline{Z}_1 = \begin{bmatrix} (5+3) & (3) \\ (3) & (4+3) \end{bmatrix}$$

$$\det \underline{Z}_1 = 47$$

$$\underline{Y}_2 = \begin{bmatrix} (\frac{1}{2} + \frac{1}{6}) & -\frac{1}{2} \\ -\frac{1}{2} & (\frac{1}{2} + \frac{1}{1}) \end{bmatrix}$$

$$\det \underline{Y}_2 = \frac{3}{4}$$

from the tables

$$\underline{T}_1 = \begin{bmatrix} \frac{8}{3} & \frac{47}{3} \\ \frac{1}{3} & \frac{7}{3} \end{bmatrix}$$

$$\underline{T}_2 = \begin{bmatrix} 3 & 2 \\ \frac{3}{2} & \frac{4}{3} \end{bmatrix}$$


$$\underline{T}_{eq} = \underline{T}_1 \underline{T}_2$$

$$\underline{T}_{eq} = \begin{bmatrix} \frac{63}{2} & \frac{236}{9} \\ \frac{9}{2} & \frac{34}{9} \end{bmatrix}$$

$$\det \underline{T}_{eq} = 1$$


from tables, we convert T_{eq} to Z_{eq}
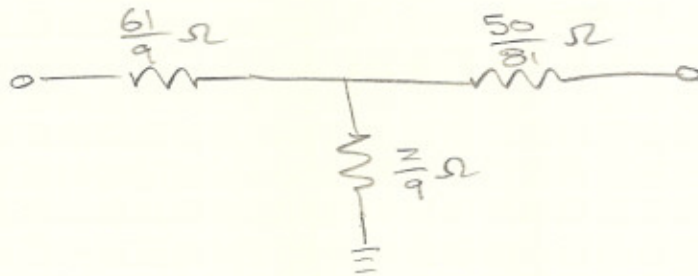
$$Z_{eq} = \begin{bmatrix} 7 & \frac{2}{9} \\ \frac{2}{9} & \frac{68}{81} \end{bmatrix}$$




SOL (method II)

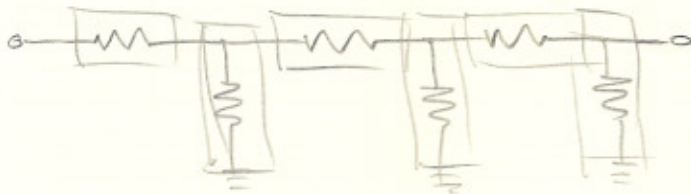this method involves the representation of each resistor as either a single series or single shunt element.



$$T_{eq} = \begin{bmatrix} 1 & 5 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{3} & 1 \end{bmatrix} \begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{6} & 1 \end{bmatrix} \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$$
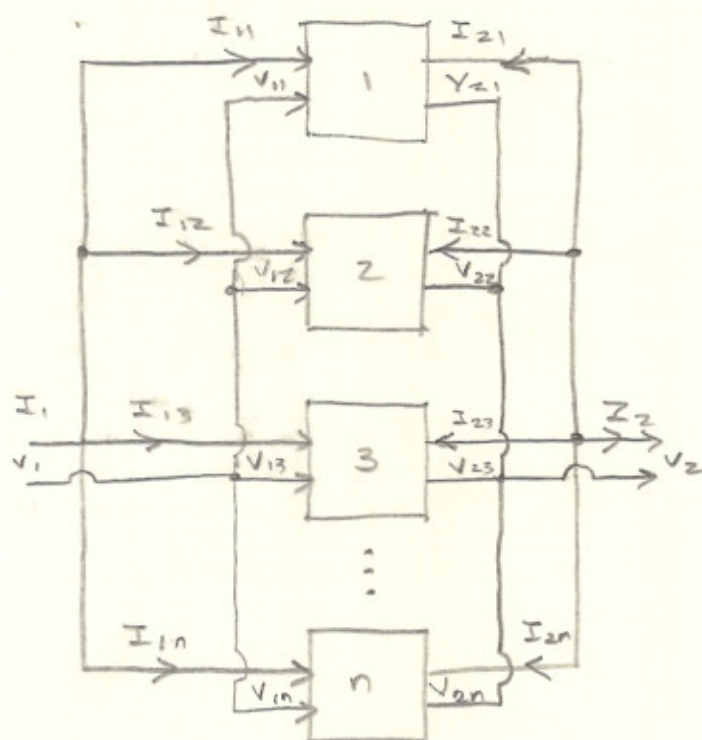
$$= \begin{bmatrix} \frac{63}{2} & \frac{236}{9} \\ \frac{9}{2} & \frac{34}{9} \end{bmatrix}$$




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_{11} \\ V_{21} \end{bmatrix} = \begin{bmatrix} V_{12} \\ V_{22} \end{bmatrix} = \begin{bmatrix} V_{13} \\ V_{23} \end{bmatrix} = \dots = \begin{bmatrix} V_{1n} \\ V_{2n} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underline{Y}_1 \begin{bmatrix} V_{11} \\ V_{21} \end{bmatrix} + \underline{Y}_2 \begin{bmatrix} V_{12} \\ V_{22} \end{bmatrix} + \underline{Y}_3 \begin{bmatrix} V_{13} \\ V_{23} \end{bmatrix} + \dots + \underline{Y}_n \begin{bmatrix} V_{1n} \\ V_{2n} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\left[\underline{Y}_1 + \underline{Y}_2 + \underline{Y}_3 + \dots + \underline{Y}_n \right]}_{\underline{Y}_{eq}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

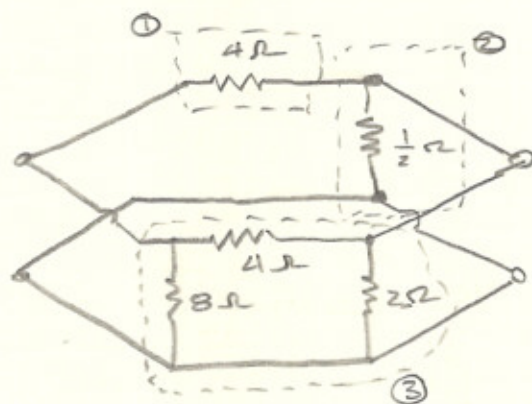Ex: obtain the equivalent h-parameter matrix for the network shown below.



STEPS

1. FROM T_1 & T_2
2. use cascade algorithm to find T_{12}
3. convert T_{12} to Y_{12}
4. form Y_3
5. form $Y_{eq} = Y_{12} + Y_3$
6. use tables to convert Y_{eq} to h_{eq}

SOL:

$$T_1 = \begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix}, \quad T_2 = \begin{bmatrix} 1 & 0 \\ 2 & 1 \end{bmatrix}$$

$$T_{12} = \begin{bmatrix} 1 & 4 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 2 & 1 \end{bmatrix} = \begin{bmatrix} 9 & 4 \\ 2 & 1 \end{bmatrix}$$

from tables

$$Y_{12} = \begin{bmatrix} \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{9}{4} \end{bmatrix}$$

$$Y_3 = \begin{bmatrix} \frac{3}{8} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{3}{4} \end{bmatrix}$$

$$\underline{Y}_{eq} = \underline{Y}_{12} + \underline{Y}_3 = \begin{bmatrix} \frac{5}{8} & -\frac{1}{2} \\ -\frac{1}{2} & 3 \end{bmatrix}$$

from tables

$$\underline{h}_{eq} = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{bmatrix}$$

$$\Delta Y = \left(\frac{5}{8}\right)(3) - \left(-\frac{1}{2}\right)\left(-\frac{1}{2}\right) = \frac{13}{8}$$

$$h_{11} = \frac{1}{Y_{11}} = \frac{8}{5}$$


$$h_{12} = -\frac{Y_{12}}{Y_{11}} = \frac{4}{5}$$

$$h_{21} = \frac{Y_{21}}{Y_{11}} = -\frac{4}{5}$$




$$h_{22} = \frac{\Delta Y}{Y_{11}} = \frac{13}{5}$$

$$\underline{H} = \begin{bmatrix} \frac{8}{5} & \frac{4}{5} \\ -\frac{4}{5} & \frac{13}{5} \end{bmatrix}$$

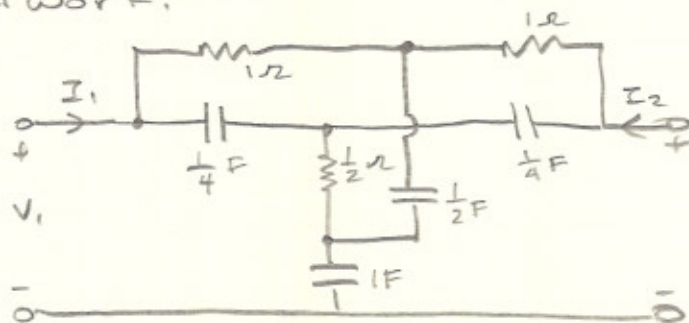Ex: Reduce the following to a single Tee network.



SOL:

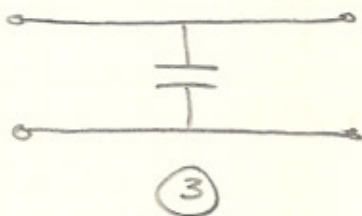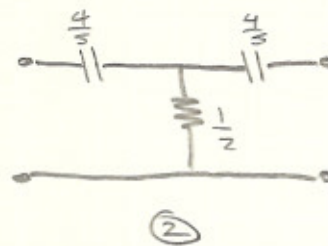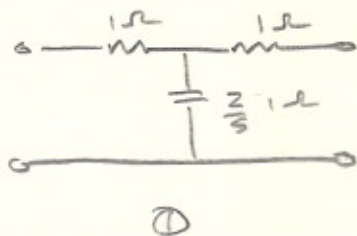

① & ② are in parallel and both are in series with the IF 2 port network, (③).

$$\underline{Z}_1 = \begin{bmatrix} 1 + \frac{2}{s} & \frac{2}{s} \\ \frac{2}{s} & 1 + \frac{2}{s} \end{bmatrix} = \begin{bmatrix} \frac{s+2}{s} & \frac{2}{s} \\ \frac{2}{s} & \frac{s+2}{s} \end{bmatrix}$$

from tables

$$\underline{Y}_1 = \frac{1}{s+4} \begin{bmatrix} s+2 & -2 \\ -2 & s+2 \end{bmatrix}$$

$$\underline{Z}_2 = \begin{bmatrix} \frac{4}{s} + \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & \frac{4}{s} + \frac{1}{2} \end{bmatrix}$$

from tables

$$\underline{Y}_2 = \frac{1}{8(s+4)} \begin{bmatrix} s^2+8s & -s^2 \\ -s^2 & s^2+8s \end{bmatrix}$$

① & ② are in parallel so...

$$\underline{Y}_{12} = \underline{Y}_1 + \underline{Y}_2$$

$$Y_{12} = \frac{1}{8(s+4)} \begin{bmatrix} s^2+16s+16 & -(s^2+16) \\ -(s^2+16) & s^2+16s+16 \end{bmatrix}$$


$Y_{12} \Rightarrow Z_{12}$ from tables

$$Z_{12} = \frac{1}{4s(s+4)} \begin{bmatrix} s^2+16s+16 & s^2+16 \\ s^2+16 & s^2+16s+16 \end{bmatrix}$$

$$Z_3 = \begin{bmatrix} \frac{1}{s} & \frac{1}{s} \\ \frac{1}{s} & \frac{1}{s} \end{bmatrix}$$

$$Z_{13} = Z_{12} + Z_3 = \frac{1}{4s(s+4)} \begin{bmatrix} s^2+16s+16 & s^2+16 \\ s^2+16 & s^2+16s+16 \end{bmatrix}$$

Hence our Tee network is

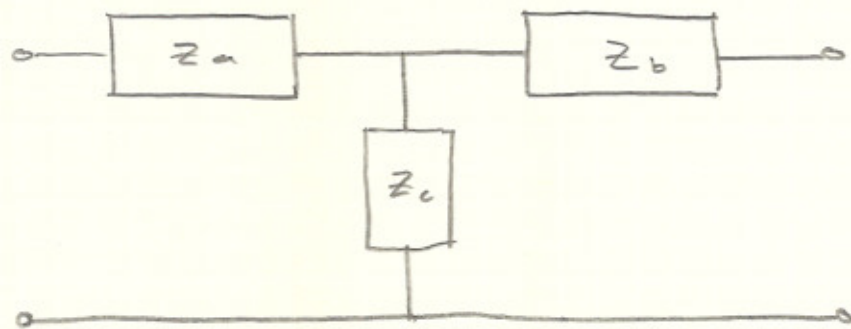

$$Z_a = Z_b = \frac{4}{s+4}$$

$$Z_c = \frac{s^2+4s+32}{4s(s+4)}$$

Reciprocity

If $Y_{21} = Y_{12}$ and $Z_{21} = Z_{12}$, then the network is said to be a reciprocal network. This means that both Y and Z are symmetrical, for a reciprocal network.

RECIPROCITY, & ABCD PARAMETERS.

consider $\begin{vmatrix} A & B \\ C & D \end{vmatrix} = AD - BC$


where $A = \frac{Z_{11}}{Z_{21}}$, $B = \frac{|Z|}{Z_{21}}$, $C = \frac{1}{Z_{21}}$, $D = \frac{Z_{22}}{Z_{21}}$

now $\begin{vmatrix} A & B \\ C & D \end{vmatrix} = \frac{Z_{11}}{Z_{21}} \frac{Z_{22}}{Z_{21}} - \left\{ \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \right\} \frac{1}{Z_{21}} = \frac{Z_{12}}{Z_{21}}$


if $Z_{12} = Z_{21}$ $|I| = 1$

CONCEPT OF SYMMETRICAL NETWORKS.


EX:

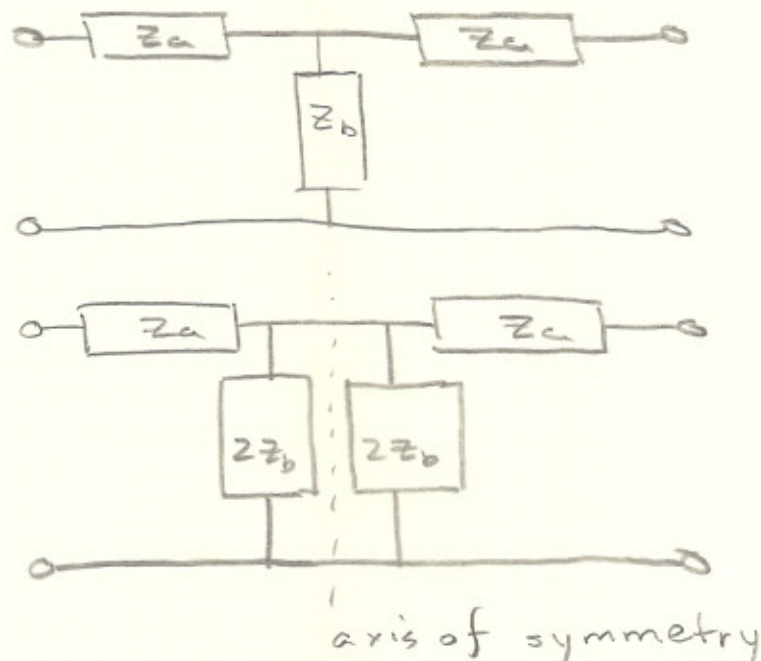

Ex:

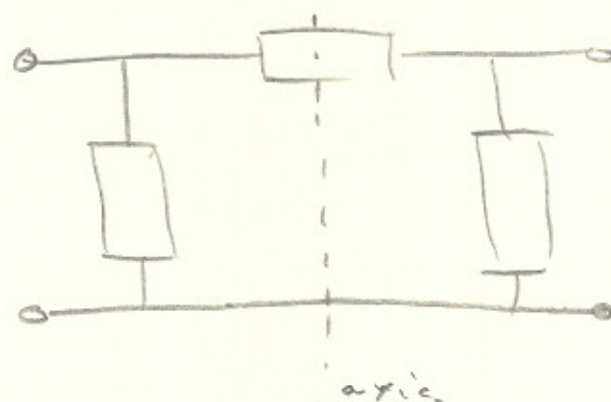

APPLICATION OF h-PARAMETERS.

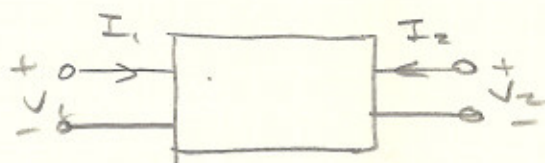

h parameters are defined as $h_i = h_{11}$, $h_r = h_{12}$, $h_f = h_{21}$ and $h_o = h_{22}$.

where, i, r, f , and o , stand for input, reverse, forward and output.

The second subscript specifies the type of connection use

e = common emitter

c = common collector

b = common base

COMMON EMITTER


h_{ie} = base input impedance.

h_{re} = reverse voltage feedback ratio

h_{fe} = Base collector current gain


h_{oe} = Output admittance.

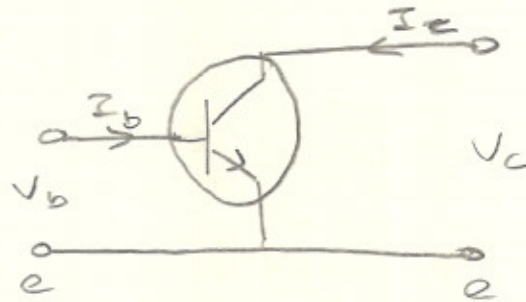The above parameters are calculated using open or closed circuit techniques, as was done earlier.



$$V_b = h_{ie} I_b + h_{re} V_c$$

$$V_c = h_{fe} I_b + h_{oe} V_c$$

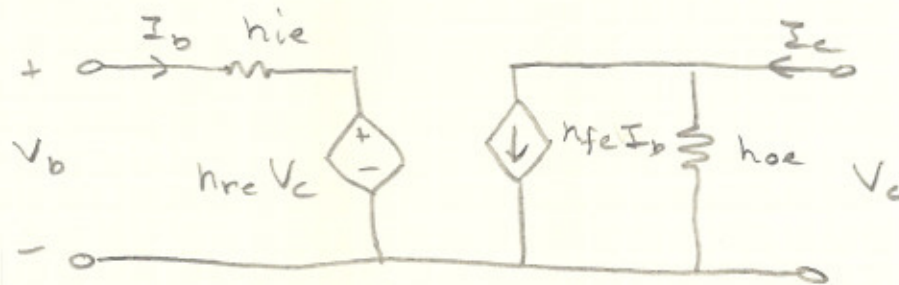

Typical values for h parameter (CE)


$$h_{ie} = 6k\Omega$$

$$h_{fe} = 200$$

$$h_{re} = 1.5 \times 10^{-4}$$

$$h_{oe} = 8\mu S$$

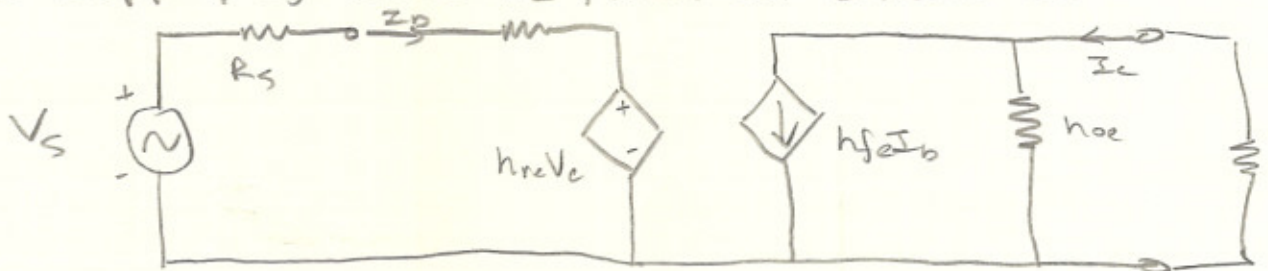if a transistor connected to an ac source, and a supply of load R_L , then our circuit is.



$$V_c = -R_c I_c$$

$$I_c = h_{fe} I_b + h_{oe} V_c$$

$$I_c = h_{fe} I_b - h_{oe} R_c I_c$$

$$(1 + h_{oe} R_c) I_c = h_{fe} I_b$$


$$A_i = \text{current gain} = \frac{I_c}{I_b}$$

$$A_v = \text{voltage gain} = \frac{V_c}{V_b}$$

$$A_i = \frac{h_{fe}}{1 + h_{oe} R_c}$$

$$A_v = \frac{-h_{fe} R_c}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_c}$$

LADDER NETWORKS

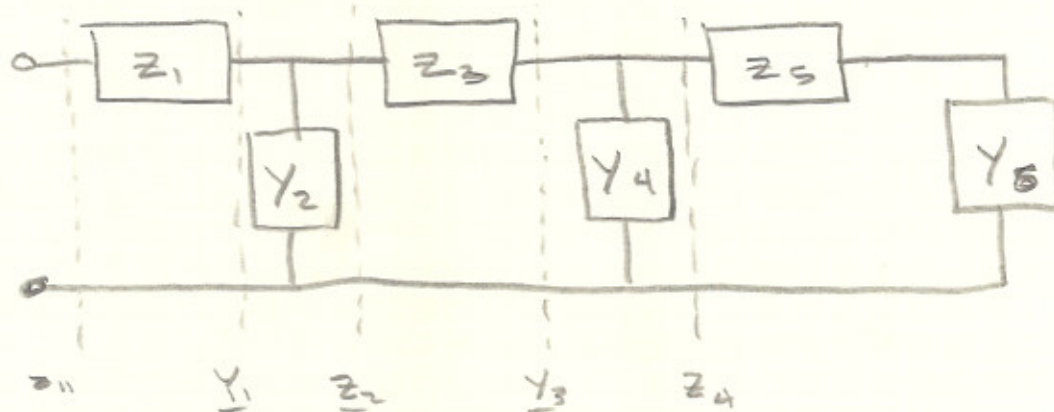

Calculating the impedance z_{11} at port ①

Impedance of the last Z arms = $z_4 = z_5 + \frac{1}{Y_6}$

admittance of the last Z arms = $Y_3 = Y_4 + \frac{1}{z_4}$

Impedance " " " 4 " = $z_2 = z_3 + \frac{1}{Y_3}$


Admittance " " " 5 " = $Y_1 = Y_2 + \frac{1}{z_2}$

Impedance " " " 6 " = $z_{11} = z_1 + \frac{1}{Y_1}$

∴

$$Z_{11} = Z_1 + \frac{1}{Y_2 + \frac{1}{Z_3 + \frac{1}{Y_4 + \frac{1}{Z_5 + \frac{1}{Y_6}}}}}$$

Ex: find z_{11} of.

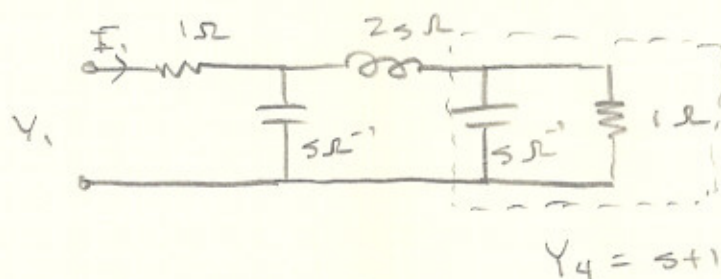

$$Z_{11} = \frac{2s^3 + 4s^2 + 4s + 2}{2s^2 + 2s^2 + 2s + 1}$$

Ex: Synthesises

$$Z(s) = \frac{2s^2 + 12s + 16}{s^2 + 4s + 3}$$

SOL:

$$\frac{s^2 + 4s + 3}{2} \overline{) 2s^2 + 12s + 16}$$

$$\underline{2s^2 + 8s + 6}$$

$$4s + 10$$

$$Z(s) = 2 + \frac{1}{\frac{s^2 + 4s + 3}{4s + 10}}$$

$$\frac{4s + 10}{Y_4 s} \overline{) s^2 + 8s + 6}$$


$$\underline{s^2 + \frac{10}{4}s}$$

$$\frac{3}{2}s + 3$$

$$Z(s) = 2 + \frac{1}{\frac{1}{4}s + \frac{1}{\frac{4s+10}{\frac{3}{2}s+3}}}$$

$$\begin{array}{r} \frac{3/2s+3}{8/3} \quad \frac{4s+10}{4s+8} \\ \hline \end{array}$$
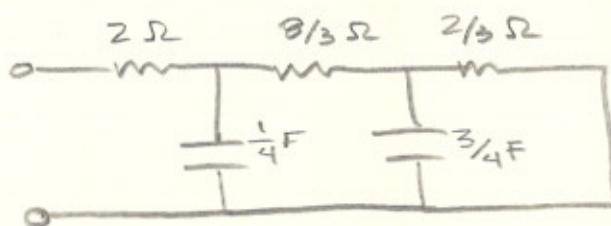
$$\therefore Z(s) = 2 + \frac{1}{\frac{1}{4}s + \frac{8/3}{\frac{3/2s+3}{2}}}$$



note: multiply back to check.

CAUR SYNTHESIS

we need to synthesise an impedance $Z(s)$ such that

$$Z(s) = k \left\{ \frac{s^m + a_{m-1}s^{m-1} + \dots + a_0}{s^n + b_{n-1}s^{n-1} + \dots + b_0} \right\}$$

or $\rightarrow \left[\frac{N(s)}{D(s)} \right] \rightarrow$ where k is positive

from the example done last, last day.

expanding the $Z(s)$ is the cover 1 network
this is easy to check, by finding the total impedance of the network.

This procedure is known as cover procedure and the network is known as cover network.

When we arrange the functions $N(s)$ & $D(s)$ in descending order, the resulting network is called a cover I network.

If $N(s)$ and $D(s)$ are arranged in ascending order, the resulting network is called a cover II network.

EX:

$$Z(s) = \frac{zs + s^3}{1 + s^3} \quad \leftarrow \text{ascending powers.}$$

find the cover II network.

SOL:

$$\begin{array}{r} 1+s^2 \overline{) 2s+s^3} \\ \underline{2s} \\ -s^2 \end{array}$$

↑ negative sign indicates that $z=0$, then

$$Z(s) = \frac{1}{\frac{1+s^2}{2s+s^3}}$$

$$\begin{array}{r|l} 2s + s^3 & 1 + s^2 \\ \hline \frac{1}{2s} & 1 + \frac{1}{2}s^2 \\ & \frac{1}{2}s^2 \end{array}$$


$$Z(s) = 0 + \frac{1}{\frac{1}{2s} + \frac{s^2}{4s + 2s^3}}$$

$$Z(s) = 0 + \frac{1}{\frac{1}{2s} + \frac{1}{\frac{4s + 2s^3}{s^2}}}$$

$$Z(s) = 0 + \frac{1}{\frac{1}{2s} + \frac{1}{\frac{4}{s} + 2s}}$$


$$Z(s) = 0 + \frac{1}{\frac{1}{2s} + \frac{4}{s} + \frac{1}{2s}}$$

the following results in

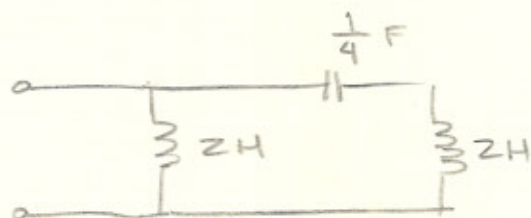

GENERAL LC CAUER NETWORKS

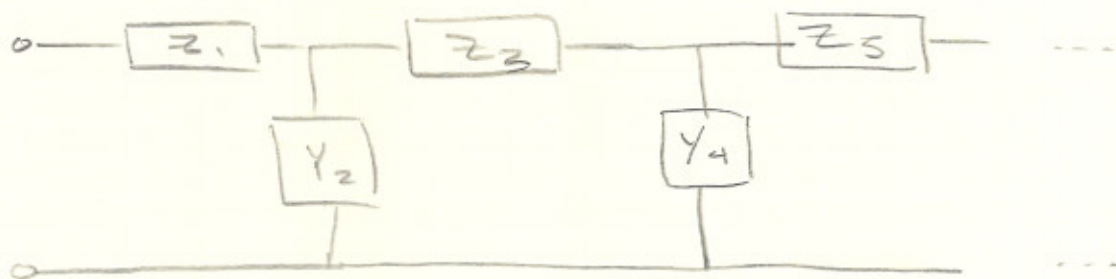there are Z networks associated with an impedance $Z(s)$ which are realizable. Cauer networks are ladder networks which have general form shown below.




$$Z = Z_1 + \frac{1}{Y_2 + \frac{1}{Z_3 + \frac{1}{Y_4 + \dots \text{etc.}}}}$$

Ex:

$$Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 9)}$$


SOL:

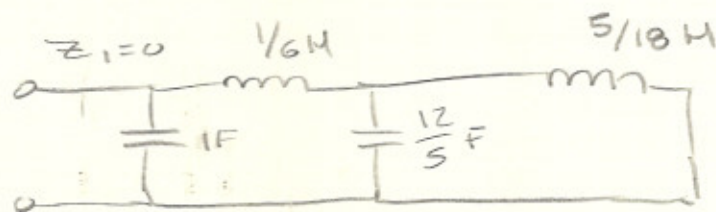

2nd cover network is obtained from:

$$Y(s) = \frac{9 + 10s^2 + s^4}{4s + s^3}$$
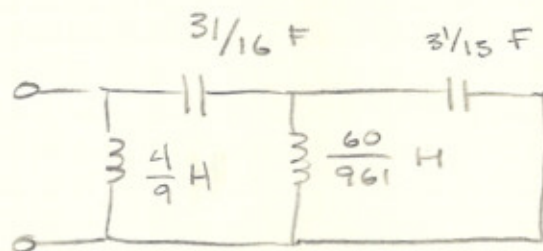
$$Y(s) = \frac{9}{4s} + \frac{1}{\frac{16}{31s} + \frac{1}{\frac{961}{60s} + \frac{1}{\frac{15}{31s}}}}$$



Ex: find Cauer realizations of

$$Z(s) = \frac{s^4 + 10s^2 + 9}{s^3 + 2s}$$

$$\frac{s^3 + 2s}{s} \overline{) \frac{s^4 + 10s^2 + 9}{s^4 + 2s^2}} \quad \underline{8s^2 + 9}$$

$$Z(s) = s + \frac{1}{\frac{s^3 + 2s}{8s^2 + 9}}$$

$$\frac{8s^2 + 9}{\frac{1}{8}s} \overline{) \frac{s^3 + 2s}{s^3 + \frac{9}{8}s}} \quad \underline{\frac{7}{8}s}$$

$$Z(s) = s + \frac{1}{\frac{1}{8}s + \frac{1}{8s^2 + 9}}$$

$$Z(s) = s + \frac{1}{\frac{1}{8}s + \frac{1}{\frac{64}{7}s + \frac{1}{\frac{7s}{72}}}}$$

