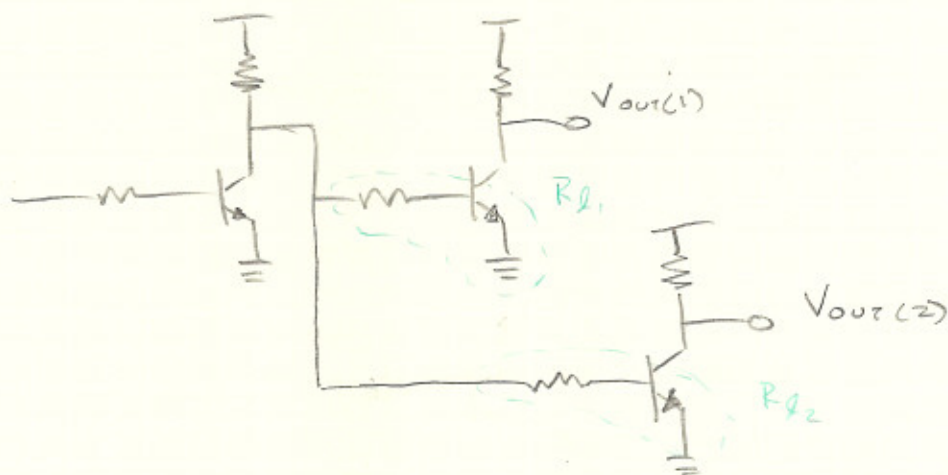


$$R_D \geq \frac{V_{out}' R_C}{V_{CC} - V_{out}'}$$


so we really don't want an R_D



$$\frac{1}{R_D} = \sum_{j=1}^n \frac{1}{R_{Dj}}$$

if R_D becomes too low, then the next stage will not operate properly.

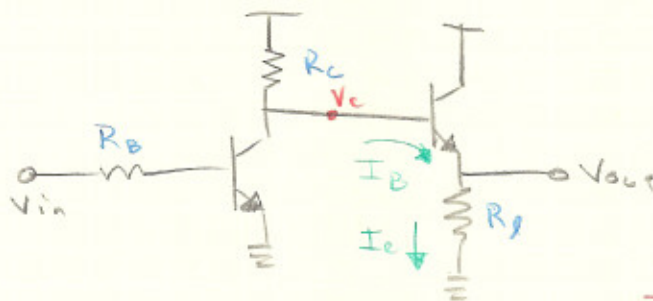so reduce this problem, we use a current driver.



T_1 is in Cut off

$$I_C = \beta I_B$$

$$I_C + I_B = I_E$$

$$\beta I_B + I_B = I_E$$

$$I_B = \frac{I_E}{1 + \beta}$$

$$V_c = V_{BE(T)} + I_e \cdot R_l$$

$$V_c = V_{cc} - I_B R_c$$

$$V_{BE(T)} + I_e R_l = V_{cc} - I_B R_c$$

$$V_{cc} + \frac{I_{E2}}{1 + \beta_2} R_c = V_{BE(T2)} + I_{E2} R_l$$

$$V_{out}' \leq V_{out} = I_{E2} R_l$$

$$V_{cc} - V_{BE(T2)} = I_{E2} \left(R_l + \frac{R_c}{1 + \beta_2} \right)$$

$$V_{out}' \leq V_{out} = \frac{V_{cc} - V_{BE(T2)}}{R_l + \frac{R_c}{1 + \beta_2}} R_l$$

$$\frac{V_{out}'}{V_{cc} - V_{BE(T2)}} \leq \frac{R_l}{R_l + \frac{R_c}{1 + \beta_2}}$$

$$\frac{V_{out}'}{V_{cc} - V_{BE(T2)}} \leq \frac{1}{1 + \frac{1}{1 + \beta_2} \cdot \frac{R_c}{R_l}}$$

$$1 + \frac{1}{1 + \beta_2} \cdot \frac{R_c}{R_l} \leq \frac{V_{cc} - V_{BE(T2)}}{V_{out}'}$$

$$\frac{R_c}{R_l} \leq \left[\frac{V_{cc} - V_{BE(T2)}}{V_{out}'} - 1 \right] (1 + \beta_2)$$


$$R_L \geq \frac{V_{out}' R_C}{V_{CC} - V_{out}' - V_{BE}(T_2)}$$

$$\left(\frac{1}{1 + \beta_2} \right)$$

$\ll 1$

hence allows us to have a much lower R_L value.

T_1 is saturation

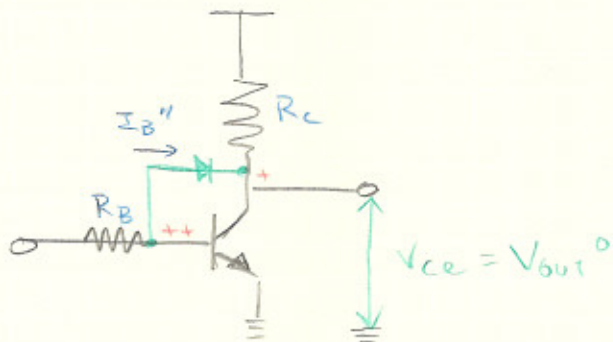

$$R_B \leq \frac{(V_{in}' - V_{CE}) \beta - R_C I_C(SAT)}{I_C(SAT)}$$

$$I_B \geq I_B' = \frac{I_C(SAT)}{\beta}$$


when we place diode, we want $V_{DT} \approx 0$

$$I_B = \frac{I_C(SAT)}{\beta} + I_B'' = I_B' + I_B''$$

when we make the diode a shotkey diode.


SCHOTTKY DIODE

Uses metal,

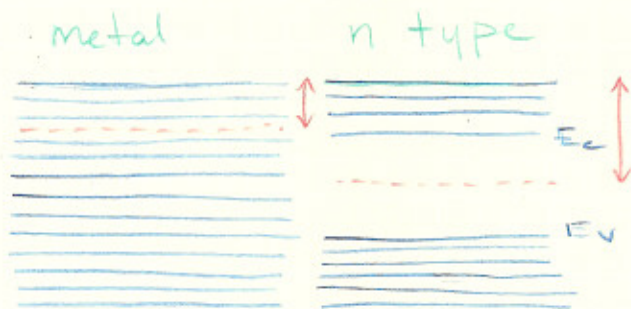


$$\phi_m < \phi_n$$

Connecting them we have

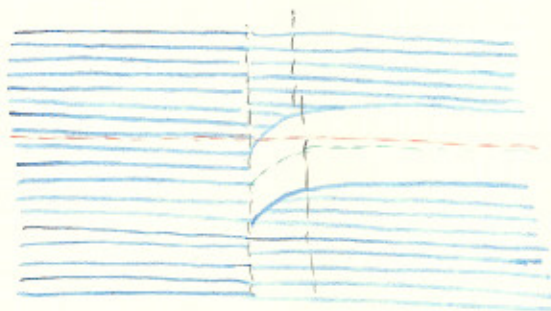

this region becomes more n

Another Case

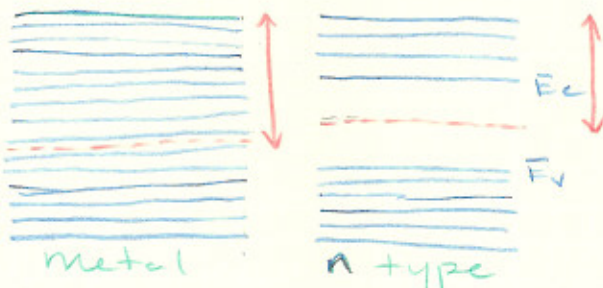

$$\phi_m > \phi_n$$

Connecting them together.

