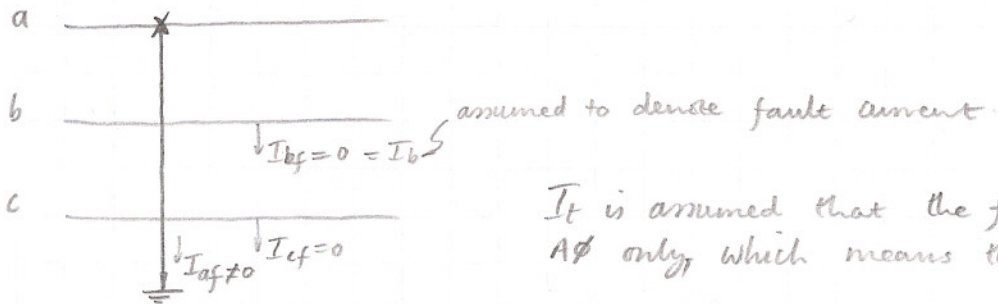


Midterm... March 9th. 1430 → 1600.

Everything up to 3 ϕ faults (ans't 1-4).

Ex Single line to ground fault... (SLG)

It is assumed that the fault is on A ϕ only, which means that:

$$I_{bf} = I_b = I_{cf} = I_c = 0.$$

$$\underline{I}_f = \begin{bmatrix} I_{af} \\ I_{bf} \\ I_{cf} \end{bmatrix} = \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix}$$

In terms of symmetrical components:

$$\begin{bmatrix} I_a \neq 0 \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_a^0 \\ I_a^+ \\ I_a^- \end{bmatrix}$$


From above, $I_{af} = I_a^0 + I_a^+ + I_a^-$

We may also write

$$\begin{bmatrix} I_a^0 \\ I_a^+ \\ I_a^- \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix} \rightarrow \text{then:}$$

$$I_a^0 = I_a^+ = I_a^- = \frac{1}{3} I_a$$

Ex 2

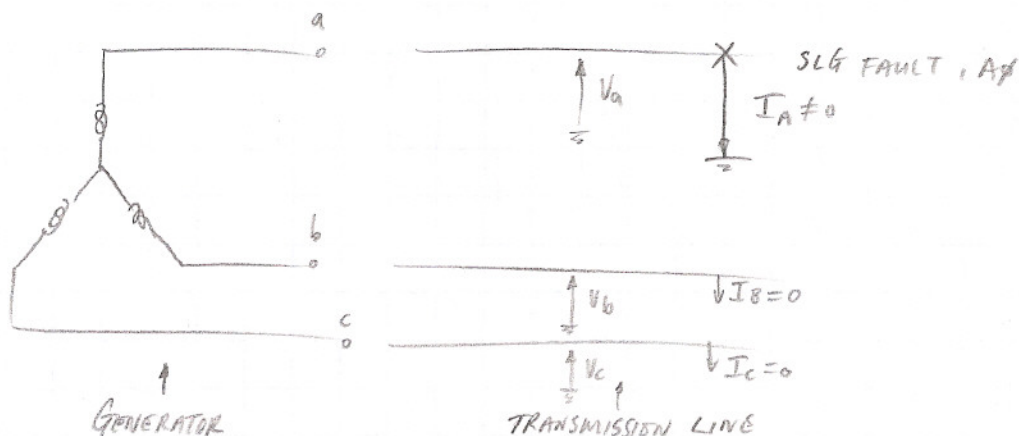

Generators operate under balanced 3 ϕ voltages which are only +ve sequence voltages. At the generator end we may write

$$\left. \begin{aligned} E_a^+ &= E_a \\ E_a^- &= 0 \\ E_a^0 &= 0 \end{aligned} \right\} \text{ due to balanced 3}\phi \text{ voltages}$$

Let us assume that the sequence impedances to the fault are Z^0 , Z^+ and Z^- . Then we may say

$$V_a^0 = 0 - Z^0 I_a^0$$

$$\uparrow$$

$$E_a^0 = 0$$

$$V_a^+ = E_a^+ - Z^+ I_a^+$$

$$V_a^- = 0 - Z^- I_a^-$$

$$\uparrow$$

$$E_a^- = 0$$

Since phase a is grounded due to the fault,

$$V_a = 0.$$

but $V_a = V_a^0 + V_a^+ + V_a^-$, and

$$0 = V_a = (-Z^0 I_a^0) + (E_a^+ - Z^+ I_a^+) + (-Z^- I_a^-)$$

NOTE:
generator voltages have
no zero or -ve seq.
components

$$0 = E_a^+ - (Z^0 + Z^+ + Z^-) I_a^0$$

$$\therefore I_a^+ = I_a^- = I_a^0 = \frac{E_a^+}{Z^0 + Z^+ + Z^-}$$

$$I_a^0 = I_a^+ = I_a^-$$

for AG-GND
(SLG) Fault.

see prev. page

In terms of phase currents...

$$I_a = \frac{3E_a^+}{Z^0 + Z^+ + Z^-}$$

$$(I_a^+ = \frac{1}{3} I_a \Rightarrow I_a = 3I_a^+)$$

$$I_b = 0$$

$$I_c = 0$$

For phase voltages, we may write

$$V_a = 0$$

$$V_b = \frac{\epsilon_b (1-\alpha) (Z^0 + (1+\alpha)Z^-)}{Z^0 + Z^+ + Z^-}$$

$$V_c = \frac{\epsilon_c (1-\alpha) ((1+\alpha)Z^+ + Z^-)}{Z^0 + Z^+ + Z^-}$$

The last two expressions can be found from


$$V_b = V_a^0 + \alpha^2 V_a^+ + \alpha V_a^-$$

$$V_c = V_a^0 + \alpha V_a^+ + \alpha^2 V_a^-$$


We may also write:

$$V_b = \frac{\alpha^2 E_a^+ - E_a^- (\alpha^2 Z^+ + \alpha Z^- + Z_0)}{Z^0 + Z^+ + Z^-}$$

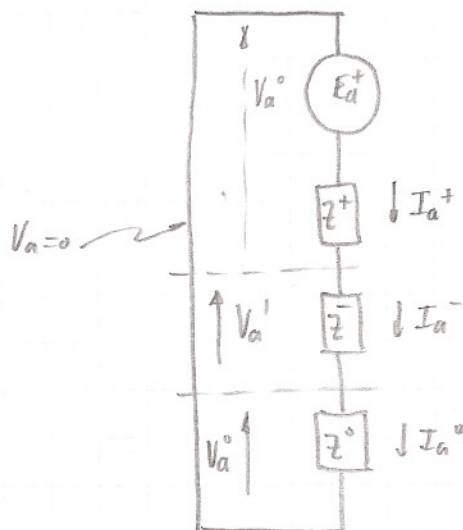Sketching the equivalent ckt for an AG SLG fault:



⇒ DLG fault

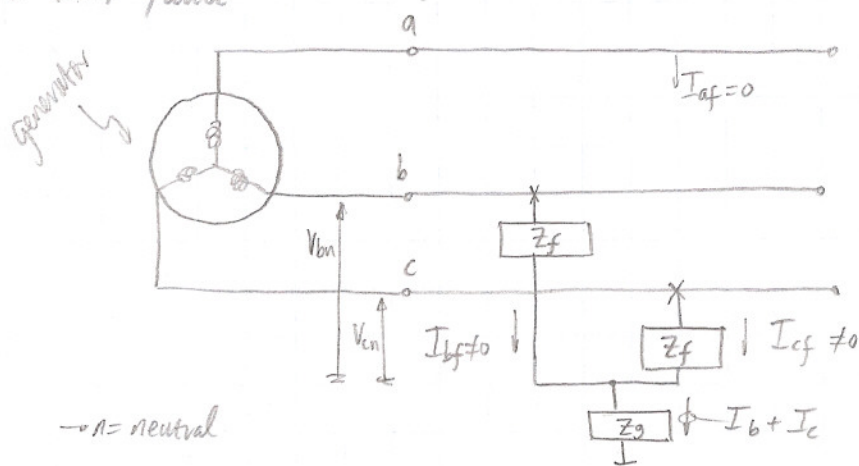

In the above, we assume that phase B has a fault impedance Z_f and phase C has also an impedance Z_f and the common branch to ground has an impedance Z_g .

From the diagram,

$$V_{cn} = I_c Z_f + (I_c + I_b) Z_g$$

$$\text{or } V_{cn} = I_b Z_g + (Z_f + Z_g) I_c$$

$$V_{bc} = V_{bn} - V_{cn} = I_b Z_f + \cancel{I_b Z_g} + \cancel{I_c Z_g} - \cancel{I_b Z_g} - I_c Z_f - \cancel{I_c Z_g}$$

$$\text{or } V_{bc} = I_b Z_f - I_c Z_f = Z_f (I_b - I_c)$$

In terms of sequence currents and voltages,

$$V_{bn} = V_b = V_a^0 + \alpha^2 V_a^+ + \alpha V_a^-$$

$$V_{cn} = V_c = V_a^0 + \alpha V_a^+ + \alpha^2 V_a^-$$

$$I_b = I_a^0 + \alpha^2 I_a^+ + \alpha I_a^-$$

$$I_c = I_a^0 + \alpha I_a^+ + \alpha^2 I_a^-$$

$$\therefore V_a^0 + \alpha^2 V_a^+ + \alpha V_a^- - V_a^0 - \alpha V_a^+ - \alpha^2 V_a^- = Z_f \{ I_a^0 + \alpha^2 I_a^+ + \alpha I_a^- - I_a^0 - \alpha I_a^+ - \alpha^2 I_a^- \}$$

$$\therefore (\alpha^2 - \alpha) V_a^+ + (\alpha - \alpha^2) V_a^- = Z_f \{ (\alpha^2 - \alpha) I_a^+ + (\alpha - \alpha^2) I_a^- \}$$

$$\text{or } (\alpha^2 - \alpha) V_a^+ - (\alpha^2 - \alpha) V_a^- = Z_f \{ (\alpha^2 - \alpha) I_a^+ - (\alpha^2 - \alpha) I_a^- \}$$

$$\therefore V_a^+ - V_a^- = Z_f (I_a^+ - I_a^-)$$

$$(A) \quad \text{or } V_a^+ - Z_f I_a^+ = V_a^- + Z_f I_a^- \quad (A)$$

Adding V_b and V_c ...

$$V_b + V_c = I_b Z_f + I_b Z_g + I_c Z_g + I_b Z_g + I_c Z_f + I_c Z_g$$

$$\text{or } V_b + V_c = (I_b + I_c) (Z_f + 2Z_g)$$

In terms of sequence quantities---

$$\alpha^2 V_a^+ + \alpha V_a^- + V_a^0 + \alpha V_a^+ + \alpha^2 V_a^- = [I_a^0 + \alpha^2 I_a^+ + \alpha I_a^- + I_a^0 + \alpha I_a^+ + \alpha^2 I_a^-](Z_f + 2Z_g)$$

Simplifying ---

D.L-G faults (cont'd)...

Simplifying ...

$$2V_a^0 + (\alpha^2 + \alpha)(V_a^+ + V_a^-) = [2I_a^0 + (\alpha^2 + \alpha)(I_a^+ + I_a^-)](Z_f + 2Z_g)$$

$$\left. \begin{aligned} (\alpha^2 + \alpha) &= -1 \\ (1 \cdot e^{j240^\circ} + 1 \cdot e^{j120^\circ}) &= -1 \end{aligned} \right\} \text{ using this, then ...}$$

$$2V_a^0 - V_a^+ - V_a^- = [2I_a^0 - I_a^+ - I_a^-][Z_f + 2Z_g], \text{ but we know that}$$

$$I_a = I_a^0 + I_a^+ + I_a^- = 0 \quad (\text{no fault on AB})^?$$

Using the above, we get

$$2V_a^0 - V_a^+ - V_a^- = 3I_a^0(Z_f + 2Z_g) \quad (B)$$

From (A), we have

$$(C) \quad V_a^- = V_a^+ - Z_f I_a^+ + Z_f I_a^- \quad (C)$$

But $I_a = 0$, then

$$0 = I_a^0 + I_a^+ + I_a^-$$

$$(D) \quad \text{or } I_a^- = -(I_a^0 + I_a^+) \quad (D)$$

(D) \rightarrow (C), we get:

$$V_a^- = V_a^+ - 2Z_f I_a^+ - Z_f I_a^0 \quad (E)$$

(E) \rightarrow (B), and simplifying, we get

$$(F) \quad V_a^0 - I_a^0(Z_f + 3Z_g) = V_a^+ - I_a^+ Z_f \quad (F)$$

We also have

$$(G) \quad V_a^+ = E_a^+ - I_a^+ Z^+ \quad (G)$$

$$(G) \quad \left. \begin{aligned} V_a^- &= -I_a^- z^- \\ V_a^0 &= -I_a^0 z^0 \end{aligned} \right\} (G)$$

(G) \rightarrow (F) and simplifying, we get

$$E_a^+ - I_a^+ (z^+ + z_f) = -I_a^0 (z^0 + z_f + 3z_g)$$

$$\text{or } E_a^+ = I_a^+ (z^+ + z_f) + \underbrace{(I_a^+ + I_a^-)}_{-I_a^0} (z^0 + z_f + 3z_g)$$

Simplifying, we get

$$(H) \quad E_a^+ = I_a^+ (z^+ + z^0 + 2z_f + 3z_g) + I_a^- (z^0 + z_f + 3z_g) \quad (H)$$

From (A), (repeated here): (A): $V_a^+ - z_f I_a^+ = V_a^- - z_f I_a^-$

then

$$E_a^+ - I_a^+ (z^+ + z_f) = -I_a^- (z^- + z_f)$$

$$(I) \therefore I_a^- = \left(\frac{I_a^+ (z^+ + z_f) - E_a^+}{z^- + z_f} \right) \quad (I)$$

From (H):

$$(J) \quad I_a^- = \frac{E_a^+ - I_a^+ (z^+ + z^0 + 2z_f + 3z_g)}{(z^0 + z_f + 3z_g)} \quad (J)$$


(I) = (J) and simplifying...

$$I_a^+ = \left[\frac{E_a^+}{(z^+ + z_f)(z^0 + z_f + 3z_g) + (z^- + z_f)(z^+ + z^0 + 2z_f + 3z_g)} \right]$$


Substitute into (J)...

We get an expression for I_a^- and I_a^0 from $I_a^0 = -(I_a^+ + I_a^-)$

From above, our equivalent circuit is

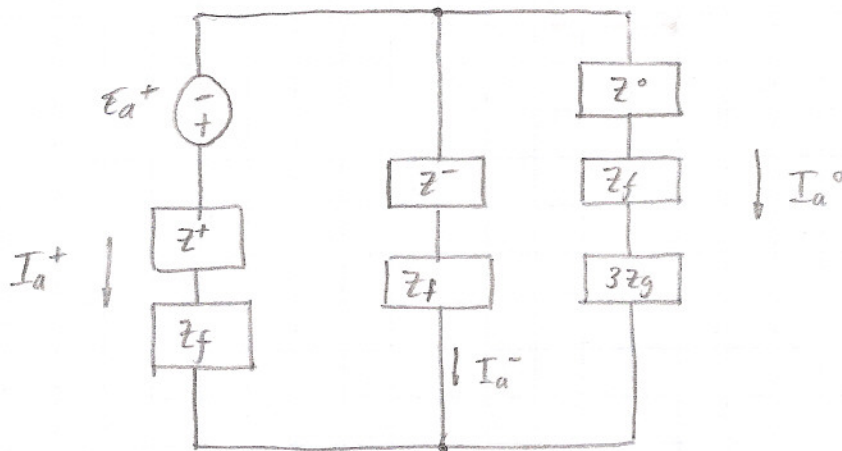

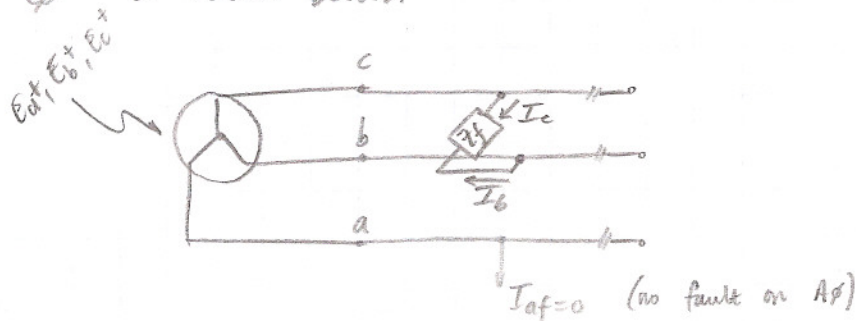
Ex Sketch the equivalent circuit for a L-L fault between Bφ and φ as shown below:



From the diagram,

- $I_b + I_c = 0 \rightarrow I_b = -I_c$
- $I_a = I_a^0 + I_a^+ + I_a^- = 0$ (fault current on Aφ = 0)

Generator voltages:

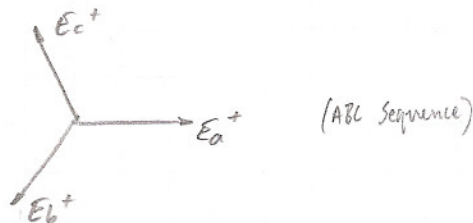

$$I_a = I_a^0 + I_a^+ + I_a^-$$

$$I_b = I_a^0 + \alpha^2 I_a^+ + \alpha I_a^-$$

$$I_c = I_a^0 + \alpha I_a^+ + \alpha^2 I_a^-$$

Since $I_b + I_c = 0 \dots$

$$(I_a^0 + \alpha^2 I_a^+ + \alpha I_a^-) + (I_a^0 + \alpha I_a^+ + \alpha^2 I_a^-) = 0$$

$$2I_a^0 + (\alpha^2 + \alpha)I_a^+ + (\alpha + \alpha^2)I_a^- = 0$$

$$2I_a^0 + I_a^+ - I_a^- = 0 \quad \checkmark \quad (I_a^0 = 0 \therefore I_a^+ = -I_a^-)$$

Actual Solution...

$$I_a = 0$$

$$I_b = -I_c$$

$$V_b - V_c = Z_f \cdot I_b$$

$$I_a = 0 = I_a^0 + I_a^+ + I_a^-$$

$$I_a^+ = \frac{1}{3} \{ I_a + \alpha I_b + \alpha^2 I_c \}$$

$$I_a^- = \frac{1}{3} \{ I_a + \alpha^2 I_b + \alpha I_c \}$$

$$I_a^+ = -I_a^- \therefore I_a^+ + I_a^- = 0$$

$$I_a^+ = -I_a^- = \frac{1}{3} (\alpha - \alpha^2) I_b$$

Voltage condition gives:

$$(\alpha^2 - \alpha)(V_a^+ - V_a^-) = Z_f (\alpha^2 - \alpha) I_a^+$$

which reduces to

$$V_a^+ - V_a^- = Z_f I_a^+$$

$$(1 \angle 240^\circ) + (1 \angle 120^\circ) = 1 \angle 180^\circ = -1$$

$I_a^0 = 0$, from matrix form...

$$\begin{pmatrix} I_a^0 \\ I_a^+ \\ I_a^- \end{pmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_a = 0 \\ I_b \\ I_c \end{bmatrix}$$

$$I_a^0 = \frac{1}{3} (0 + 0 + 0) = 0, \quad I_b = -I_c \therefore I_a^0 = \frac{1}{3} (0) = 0$$

since $I_a^0 = \frac{1}{3} \{ I_a + I_b + I_c \}$

and $\frac{I_a + I_b + I_c}{0} = 0,$


$I_a^0 = 0$

$$\frac{1}{3} (\alpha I_b + \alpha^2 I_c) - \frac{1}{3} (\alpha^2 I_b + \alpha I_c)$$

$$\frac{1}{3} [(\alpha - \alpha^2) I_b + (\alpha^2 - \alpha) I_c]$$

$$\frac{1}{3} [(\alpha - \alpha^2) I_b + (-\alpha + \alpha^2) I_c] = 0 \therefore I_b = -I_c$$

The equivalent ckt. is:

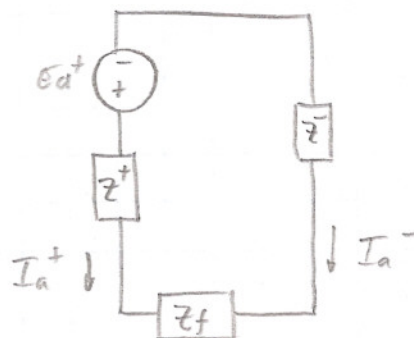

⇒ Power in terms of symmetrical components...

Complex power (3ϕ) is given by

$$\begin{aligned}\bar{S}_{3\phi} &= P_{3\phi} + j Q_{3\phi} \\ &= \bar{V}_a \bar{I}_a^* + \bar{V}_b \bar{I}_b^* + \bar{V}_c \bar{I}_c^* \\ &= [\bar{V}_a \ \bar{V}_b \ \bar{V}_c] \begin{bmatrix} \bar{I}_a^* \\ \bar{I}_b^* \\ \bar{I}_c^* \end{bmatrix} = \begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix}^T \begin{bmatrix} \bar{I}_a^* \\ \bar{I}_b^* \\ \bar{I}_c^* \end{bmatrix}\end{aligned}$$

But we have

$$\underline{V}_s = \begin{bmatrix} V_a^0 \\ V_a^+ \\ V_a^- \end{bmatrix}, \quad \underline{I}_s = \begin{bmatrix} I_a^0 \\ I_a^+ \\ I_a^- \end{bmatrix}$$

$$\text{and } \underline{V} = [V_a \ V_b \ V_c]^T \quad \underline{I} = [I_a \ I_b \ I_c]^T$$

From $\underline{V} = \underline{A} \underline{V}_s$ and $\underline{I} = \underline{A} \underline{I}_s$, then:

$$\begin{aligned}\bar{S}_{3\phi} &= (\underline{V})^T \cdot \underline{I}^* \\ &= [\underline{A} \underline{V}_s]^T [\underline{A} \underline{I}_s]^*\end{aligned}$$

$$[\underline{A} \underline{V}_s]^T = [\underline{V}_s]^T [\underline{A}]^T$$

$$(\underline{A} \underline{I}_s)^* = \underline{A}^* \underline{I}_s^*$$

$$\bar{S}_{3\phi} = \underline{V}_s^T \underline{A}^T \underline{A}^* \underline{I}_s^*$$

$$\underline{A} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}$$

$$\underline{A}^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix}$$

$$[\underline{A}][\underline{A}^*] = \frac{1}{3}.$$