



$$V_{3f} = -17.72 \cdot 0.6209 = -11V$$

$$I_{12f} = \frac{-3.14 - (-6.28)}{1} = 3.14 A$$

$$I_{2gf} = \frac{-6.28 - 0}{4} = -1.57 A$$

$$I_{23f} = \frac{-6.28 - (-11)}{1} = 4.72 A$$

$$I_{G11f} = \frac{0 - (-3.14)}{1} = 3.14 A$$

$$I_{G23f} = \frac{0 - (-11)}{1} = 11 A$$

$$I_{120} = \frac{11.5 - 10}{1} = 1.5 A$$

$$\therefore I_{12} = I_{120} + I_{12f}$$

$$= 1.5 + 3.14 = 4.64 A.$$

$$V_1 = V_{10} + V_{1f} = 11.5 + (-3.14) = 8.36 V$$

$$V_2 = V_{20} + V_{2f} = 10 + (-6.28) = 3.72 V$$

$$V_3 = V_{30} + V_{3f} = 11 + (-11) = 0 V$$

Note: One the  $Z_{bus}$  (or column of it) is found the solution for the fault voltages and current flows immediately


Note: If the fault occurs on bus #2 (to ground) then the fault at bus 2 is

$$I_f = \frac{-10}{0.7742} = -12.92A$$

Note: the prefault voltages are generally obtained from the load flow solution of the system, for this load flow solution; an admittance matrix  $Y_{bus}$  is known. This matrix however omits generator and load branch impedances. To form the  $Y_{bus}$ , all is necessary is to add generator and load admittances to the diagonal elements of  $Y_{bus}$

$$Y_{bus} = Y_{bus} + \begin{bmatrix} \text{diagonal} \\ \text{source and} \\ \text{Load} \\ \text{admittances} \end{bmatrix}$$

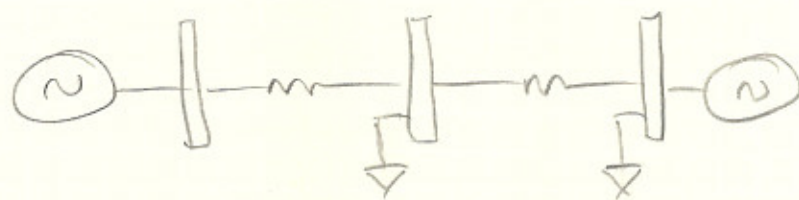EX: Building up your  $Y_{bus}$  for the previous example.




$$Y_{bus} = \begin{bmatrix} 1 & -1 & 0 \\ -1 & 2 & -1 \\ 0 & -1 & 1 \end{bmatrix}$$

Including source and load admittances, then

$$\underline{Y}_{bus} = \begin{bmatrix} 1 & -1 & 0 \\ -1 & 2 & -1 \\ 0 & -1 & 1 \end{bmatrix} + \begin{bmatrix} 1 & 0 & 0 \\ 0 & 0.25 & 0 \\ 0 & 0 & 1.18 \end{bmatrix}$$
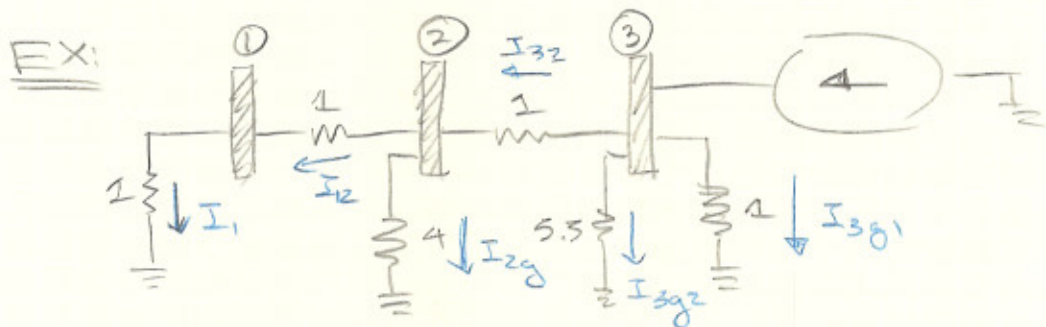
## BUILDING ZBUS

The terms of  $Z_{bus}$  can also be found directly by injecting a current into each bus in turn finding the corresponding bus voltages



let  $I_1 = 1$  *could be any value.*

$$V_1 = 1$$

$$I_{12} = 1$$

$$V_2 = 2V$$

$$I_{2g} = 0.5A$$

$$I_{32} = 1.5A$$

$$V_3 = 2 + 1.5 = 3.5V$$

$$I_{3g2} = 0.64A$$

$$I_{3g1} = 3.5A$$

$$I_3 = 5.64A$$


$$\therefore \frac{V_1}{I_3} = Z_{13} = 0.1774$$

$$\frac{V_2}{I_3} = Z_{23} = 0.3548$$



$$i. \quad \frac{V_3}{S_3} = Z_{33} = 0.6210$$

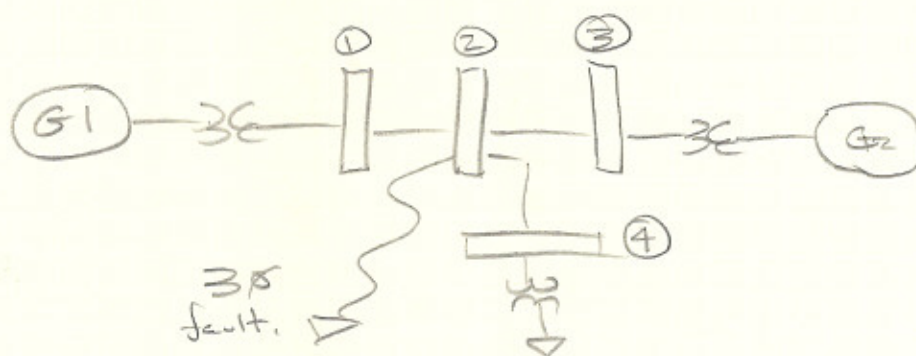EX: Given the following, determine the system voltages and currents for a 3 $\phi$  fault on bus #2, solve directly without the use of  $Z_{bus}$  method.



$$Z_{12} = Z_{23} = Z_{24} = j0.1 \text{ pu}$$

$$Z_{G1} = Z_{G2} = j0.3 \text{ pu}$$

$$Z_{T1} = Z_{T2} = Z_{T3} = j0.1 \text{ pu}$$

prefault load flow solution gave

	V	S
1	$1.06 + j0.12$	$0.4 + j0.26$
2	$1.04 + j0.08$	$0 + 0j$
3	$1.06 + j0.12$	$0.4 + j0.26$
4	$1 + 0j$	$-0.8 - j0.4$