

continued from last day,

$$\underline{I}_A = \underline{K} \underline{V}_A + \underline{L} \underline{V}_x \quad (1)$$

$$\underline{I}_x = \underline{L}^T \underline{V}_A + \underline{M} \underline{V}_x \quad (2)$$

$$\underline{I}_x = 0$$

$$(2) \Rightarrow \underline{L}^T \underline{V}_A = -\underline{M} \underline{V}_x \quad (3)$$

$$\underline{V}_x = -\underline{M}^{-1} \underline{L}^T \underline{V}_A \quad (4)$$

$$(4) \rightarrow (1) \quad \underline{I}_A = \underline{K} \underline{V}_A - \underline{L} \underline{M}^{-1} \underline{L}^T \underline{V}_A$$


$$\underline{I}_A = \boxed{\underline{K} - \underline{L} \underline{M}^{-1} \underline{L}^T} \underline{V}_A$$

\underline{Y}_{new}

This ladder equation enables us to construct the network with the unwanted nodes eliminated.

Matrix partitioning is convenient but it requires to invert the submatrix \underline{M} , which can be a large matrix. To avoid inverting \underline{M} , elimination can be carried out by eliminating one node at a time, making the process very simple.

EX:

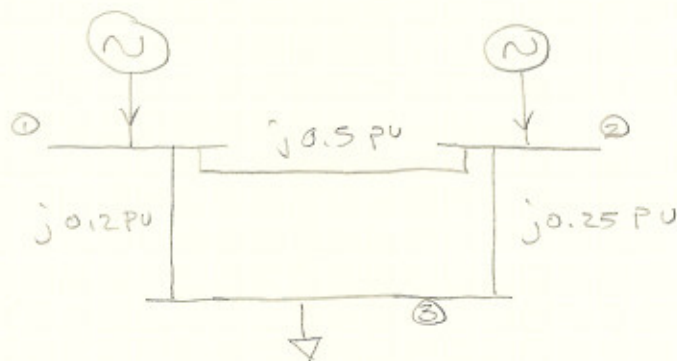

form the Y_{bus} , find the new Y_{bus} by eliminating node #3 2

SOL

$$Y_{bus} = \begin{bmatrix} -j7.0 & j2 & j5 \\ j2 & -j6 & j4 \\ j5 & j4 & -j9 \end{bmatrix}$$

$$\begin{bmatrix} \underline{I}_n \\ \underline{I}_x \end{bmatrix} = \begin{bmatrix} \underline{K} & \underline{L} \\ \underline{L}^T & \underline{M} \end{bmatrix} \begin{bmatrix} V_A \\ V_x \end{bmatrix}$$

in our case we have

$$\begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \\ 0 \end{bmatrix} = \begin{bmatrix} -j7 & j2 & j5 \\ j2 & -j6 & j4 \\ j5 & j4 & -j9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\therefore (Y_{bus})_{new} = [\underline{K} - \underline{L} \underline{M}^{-1} \underline{L}^T]$$

$$= j \begin{bmatrix} -7 & 2 \\ 2 & -6 \end{bmatrix} - j \begin{bmatrix} 5 \\ 4 \end{bmatrix} \left(\frac{1}{j9} \right) j \begin{bmatrix} 5 & 4 \end{bmatrix}$$

$$= j \left[\begin{bmatrix} -7 & 2 \\ 2 & -6 \end{bmatrix} + \frac{1}{9} \begin{bmatrix} 25 & 20 \\ 20 & 25 \end{bmatrix} \right]$$

$$= j \begin{bmatrix} -4.222 & 4.222 \\ 4.222 & -4.222 \end{bmatrix}$$

note: It will be symmetrical, but not necessarily the same values

LOAD FLOW PROBLEM

Basically a load flow study is the solution of a system for relevant voltages, phase angles and active/reactive power flows, given specified loads and operating limits on the system.

From this data, satisfactory or unsatisfactory operation with respect to line flows and voltage levels can be found and variations in system operation, addition and deletion of lines can be studied.

A basic load flow may be modified to minimize operating costs and maximize reliability and provide a starting point for

"What happens if..." explorations

SYSTEM EQUATIONS

the basic equations relating voltage and current in a system, may be expressed by loop, node, or mixed equations.

Here in this course, we shall only use the nodal formulation as it has several advantages. These include quick, easy selection of proper equations and sparsity of the resulting admittance matrix.

A sparse matrix is one in which most of the off-diagonal elements are zero. This is an advantage in Programming as it saves time and storage.