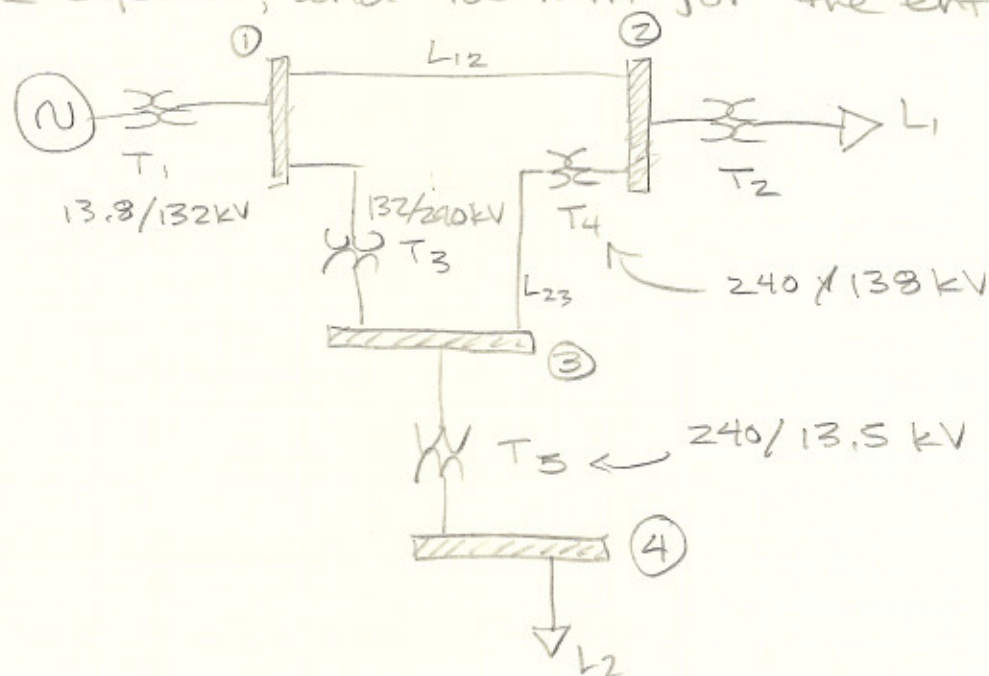


#1

Determine the PU impedance diagram of the following power system... choose base voltage of 250 kV on bus #3 for the HV side of the system, and 100 MVA for the entire system.



System information

Unit	Rated kV	Rated MVA	Z_{pu}	Z_r
G_1	14.0	150	$j0.2$	
T_1	13.8/132	150	$j0.1$	
T_2	138/13.8	75	$j0.1$	
T_3	132/240	75	$j0.1$	
T_4	240/138	75	$j0.1$	
T_5	240/13.5	50	$j0.1$	
L_{12}	138			$j25\Omega$
L_{23}	240			$j50\Omega$

note: use transformation ratios to go from one base to another

BUS # 3

$$V_{base} = 250 \text{ kV}$$

BUS # 1

$$V_{base} \cdot \frac{132}{240} \cdot 250 = 137.5 \text{ kV}$$

BUS # 2

$$V_{base} \cdot \frac{138}{240} \cdot 250 = 143.8 \text{ kV}$$

GEN G_1

$$V_{base} \cdot \frac{13.8}{132} \cdot 137.5 = 14.4 \text{ kV}$$

BUS # 4

$$V_{base} \cdot \frac{13.5}{240} \cdot 250 = 14.1 \text{ kV}$$

LOAD # 1

$$V_b \cdot \frac{13.8}{138} \cdot 143.8 = 14.4 \text{ kV}$$

for the 240 kV V_b part of the system.

$$Z_b = \frac{(250 \text{ kV})^2}{100 \text{ MVA}} = 625 \Omega$$

yielding

$$Z_{L23} = \frac{j50 \Omega}{625 \Omega} = j0.08 \text{ PU.}$$

$$Z_{T3} = j0.1 \left(\frac{240}{250} \right)^2 \left(\frac{100}{50} \right) = j0.123 \text{ PU}$$

$$Z_{T4} = j0.123 \text{ PU}$$

$$Z_{T5} = (j0.1) \left(\frac{240}{250} \right)^2 \left(\frac{100}{50} \right) = j0.184 \text{ pu}$$

$$L_{12} \Rightarrow Z_{12} = \frac{j25}{\left(\frac{137.5^2}{100 \text{ MVA}} \right)} = j0.132 \text{ pu}$$

* 137.5 kV is the voltage of bus #1 *


$$G_1 \Rightarrow Z_{G1} = (j0.2) \left(\frac{14}{14.4} \right)^2 \left(\frac{100}{150} \right) = j0.126 \text{ pu}$$

$$Z_{T1} = (j0.1) \left(\frac{132}{137.5} \right)^2 \left(\frac{100}{150} \right) = j0.06 \text{ pu}$$

$$Z_{T2} = (j0.1) \left(\frac{138}{143.8} \right)^2 \left(\frac{100}{75} \right) = j0.123 \text{ pu}$$


A problem remains at T_4 on the LV side of T_4 is not the same as that of bus #2. Based on the fact that L_{12} carries the same base from bus #1. If the connection is open as shown below, there will exist a voltage difference of $(143.8 - 137.5) \text{ kV} = 6.3 \text{ kV} = \Delta V$, or voltage difference.
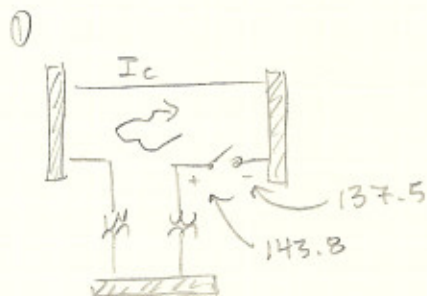
$$\frac{6.3 \text{ kV}}{143.8 \text{ kV}} = 0.044 \text{ pu}$$




If the circuit is closed a circulating current will form.

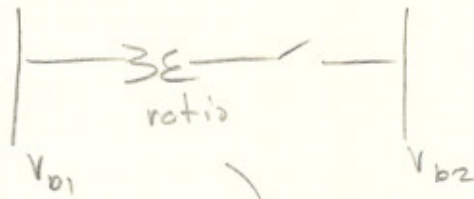
Both the secondary of the transformer and the bus are at 1.0 pu. This circulating current can be represented as an autotransformer.



$$\frac{V_{b1}}{a - V_{b2}}$$

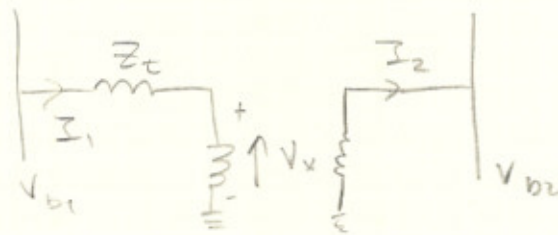

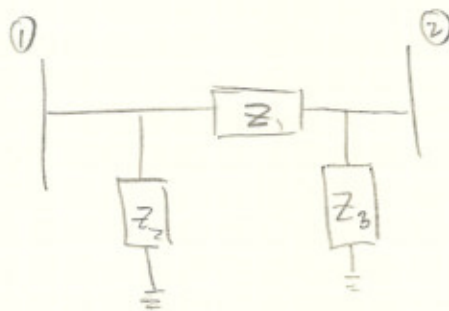this is an awkward alternative ckt. using a voltage and a current source shown below can be more conveniently represented by a π network.



The π network has passive elements only, so it is easy to include in the bus impedance or admittance matrix.

$$Z_1 = a Z_T$$

$$Z_2 = \frac{a Z_T}{(a-1)}$$

$$Z_3 = \frac{a^2 Z_T}{(1-a)}$$

The final PU impedance diagram is:

