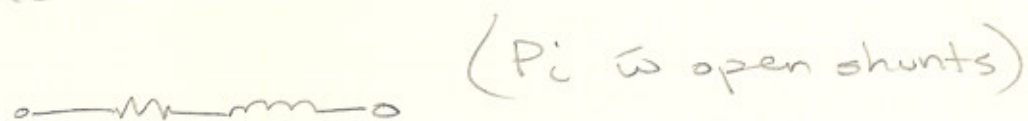


short line




medium line



TRANSFORMERS (P.U. system)

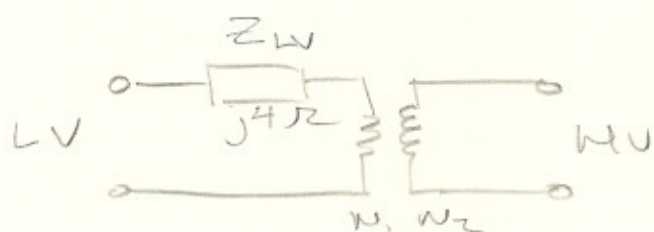consider the following transformer system w/ all series impedances referred to the low voltage side



let us assume that the transformer is rated @ 200/400V and 2000 VA, and choose base quantities to be rated quantities.

find primary PU impedances of the transformer

- low voltage side
- high voltage side.

$$Z_b = \frac{V_b}{I_b} \cdot \frac{V_b}{V_b} = \frac{V_b^2}{VA_b}$$

$$(Z_{xmer})_{pu} = \frac{Z_{\Omega}}{Z_b}$$

$$\left. \begin{array}{l} (VA)_b = 2000 \text{ VA} \\ V_b = 200 \text{ V} \end{array} \right\} \text{ LV side.}$$

then

$$I_b = \frac{2000}{200} = 10 \text{ A}$$

$$Z_b = \frac{200}{10} = 20 \Omega$$

Impedance of transformer (LVS) is

$$Z_{pu} = \frac{Z_{\Omega}}{Z_b} = \frac{j4\Omega}{20} = 0.2j \text{ pu.}$$

Referred to the high voltage side

$$(Z_{xmer})_{HV} = \left(\frac{N_2}{N_1} \right)^2 Z_{LV} = 2^2 4j = 16j \Omega$$


$$\left. \begin{array}{l} (VA)_b = 2000 \text{ VA} \\ V_b = 400 \text{ V} \end{array} \right\} \text{ HVS}$$

$$I_b = \frac{2000}{400} = 5 \text{ A}$$

$$Z_b = \frac{400}{5} = 80 \Omega$$

$$(Z_{pu})_{HVS} = 0.2j \text{ pu.}$$

∴ the equivalent ckt of the Xmer is thus


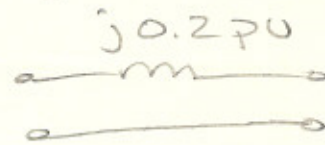


LINES & CABLES

$$Z_{pu} = \frac{Z_{ohm}}{Z_b} = Z_{ohm} \left(\frac{(VA)_b}{V_b^2} \right)$$

EX: Given the following 10 kVA transformer
w impedance referred to

- HVS
- LVS

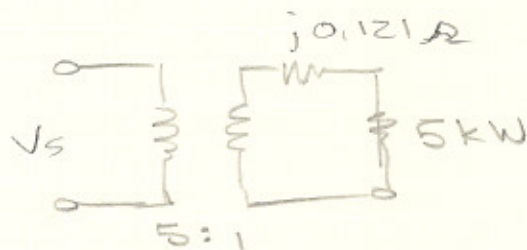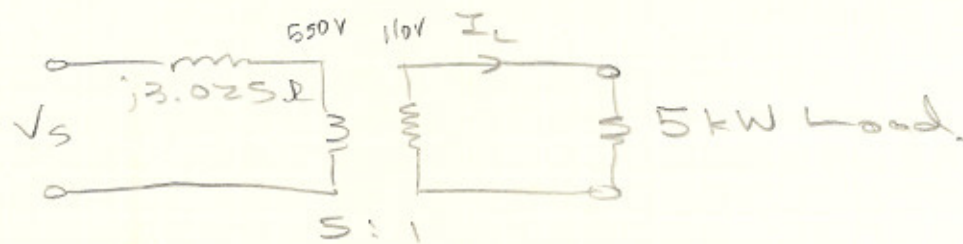

determine and sketch the PU impedance diagram choosing the transformer rating to be our base quantities.

SOL: HVS

$$V_b = 550 \text{ V}$$

$$(VA)_b = 10^4 \text{ VA}$$

$$Z_b = \frac{(550)^2}{10^4} = 30.25 \Omega$$

$$I_b = \frac{(VA)_b}{V_b} = \frac{10^4}{550} = 18.18 \text{ A}$$

$$(Z_{xmer})_{pu} = j \frac{3.025}{30.25} = 0.1j \text{ pu}$$

load (a) 5kW, 550V and 1.0 pF

$$P_{LOAD} = \frac{5000}{10^4} = 0.5 \text{ pu}$$

$$I_{pu} = \frac{0.5}{V_{pu}} = 0.5$$


$$I_{ACT} = 0.5 \times 18.18 = 9.09 \text{ A.}$$

Voltage behind transformer leakage reactance is then
where V_{pu} is in pu

$$V_{pu} = 1.0 + j 0.1(0.5)$$

$$V_{actual} = 550(1.0 + 0.05j) \\ = 550 + j 27.5 \text{ V}$$

PU impedance diagram.

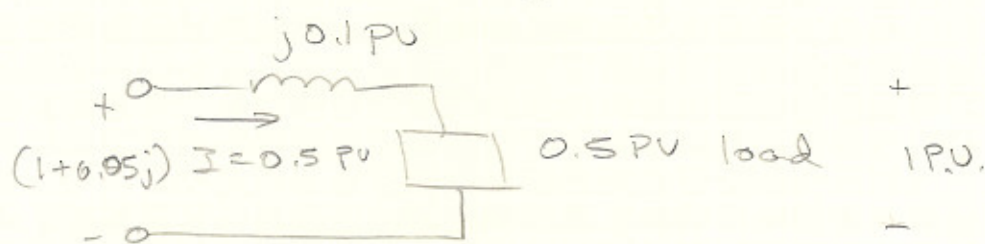

SOL: LVS

$$V_b = 110 \text{ V}$$

$$(VA)_b = 10^4 \text{ VA}$$

$$Z_b = 1.21 \Omega$$

$$I_b = 90.91 \text{ A}$$

load in P.U.

$$\frac{5000}{10^4} = 0.5$$

load voltage in PU

$$\frac{110}{110} = 1.0 \text{ PU}$$

current in PU

$$I_{act} = 45.45$$

$$\frac{0.5}{1} = 0.5 \text{ PU}$$

voltage behind reactance

$$V_{ps} = 1.0 + j0.1(0.5)$$

$$V_{act} = 110(1.0 + j0.05) = 110 + j5.5 \text{ V}$$

diagram will remain the same.