

PU

in general, the impedance of a generator, motor or transformer is given in PU or percentage based on the machines ratings.

to convert a PU impedance from an old base to a new base, we use the following equation

$$(Z_{PU})_{NEW} = (Z_{PU})_{OLD} \frac{(V_b)_{OLD}^2}{(V_b)_{NEW}^2} \cdot \frac{[(MVA)_b]_{NEW}}{[(MVA)_b]_{OLD}}$$


EX: A transformer is rated at 100 KV/25KV, 100 MVA and has a reactance of 10%. Choose a base voltage of 110 KV on the primary side of the transformer and a base MVA of 50 MVA.

find the PU impedance of the transformer.

SOL:

$$\begin{aligned} (Z_{PU})_{NEW} &= j0.1 \cdot \left(\frac{100}{110}\right)^2 \cdot \frac{50}{100} \\ &= j0.041322 \text{ PU} \end{aligned}$$

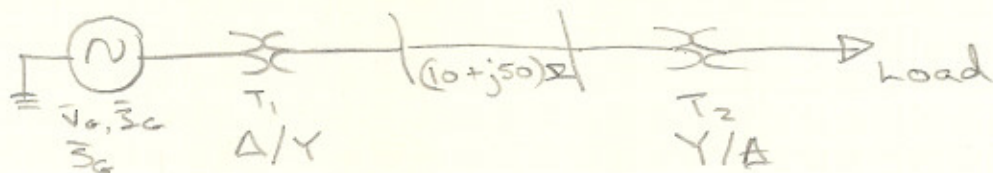EX: Solve the system shown below for \bar{I}_G , \bar{V}_G and \bar{S}_G using the PU concept.



T_1 : 100 MVA, 13.8/138 KV, $z = j0.1$ PU.

T_2 : 75 MVA, 138/14 KV, $z = j0.1$ PU.

Load: 50 MVA, 13.5 KV, Y connected, 0.8 PF lg.

SOL: let us choose a base voltage on the high voltage side. of T_1

$$\begin{aligned}(V_b)_{HVS} &= 138 \text{ kV} \\ (V_b)_{LVS} &= 13.8 \text{ kV}\end{aligned} \quad \left. \vphantom{\begin{aligned}(V_b)_{HVS} &= 138 \text{ kV} \\ (V_b)_{LVS} &= 13.8 \text{ kV}\end{aligned}} \right\} \text{ for } T_1$$

$$(V_b)_{\text{LOAD}} = 14 \text{ kV}$$

now choose a convenient base for MVA.

$$(MVA)_b = 100 \text{ MVA}$$

$$\therefore (Z_b)_{HVS} = \frac{138^2}{100} = 190.4 \Omega$$

$$(Z_{\text{LINE}})_{\text{PU}} = \frac{10 + 50j}{190.4} = 0.0525 + j0.2626$$

$$(Z_{T1})_{\text{PU}} = \text{remains the same} = 0.1j \text{ PU.}$$

$$(Z_{T2})_{\text{PU}} = j0.1 * \left(\frac{138}{13.8}\right)^2 * \frac{100}{75} = j0.13333,$$

$$(V_{\text{LOAD}})_{\text{PU}} = \frac{13.5}{14} = 0.964 \text{ PU}$$

$$|\bar{S}_{\text{LOAD}}| = \frac{50}{100} = 0.5 \text{ PU.}$$

$$(\bar{S}_{\text{LOAD}})_{\text{PU}} = 0.5(0.8 + j0.6)$$

$$(\bar{I}_G)_{\text{PU}} = \frac{(\bar{S}_G^*)_{\text{PU}}}{(\bar{V}_G^*)_{\text{PU}}} = \frac{0.5(0.8 + j0.6)}{0.964}$$

$$= 0.415 - j0.311$$

$$(\bar{V}_G)_{\text{PU}} = \frac{0.964 \angle 0^\circ}{\text{ref.}} + (0.415 - j0.311)(0.0525 + j0.2626 + j0.1 + j0.13333)$$

$$= 1.14 + j 0.189$$


$$= 1.156 \angle 9.4^\circ \text{ PU}$$

Line Voltage in P.U.

$$(V_G)_{LL} = (13.8)(1.156) = 15.95 \text{ kV}$$

Actual.

HWK:

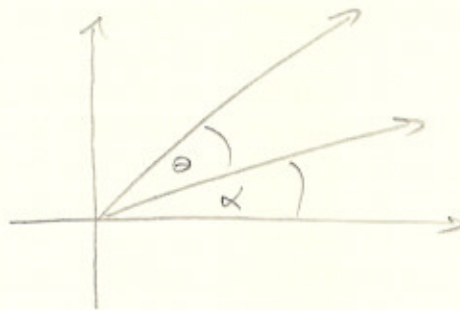


$$\bar{V} = |\bar{V}| e^{j\alpha}$$

$$\bar{I} = |\bar{I}| e^{j(\alpha + \theta)}$$

$$\bar{S} = \bar{V} \bar{I}^*$$


NETWORK CALCULATIONS.

Thevenin/Norton transformation

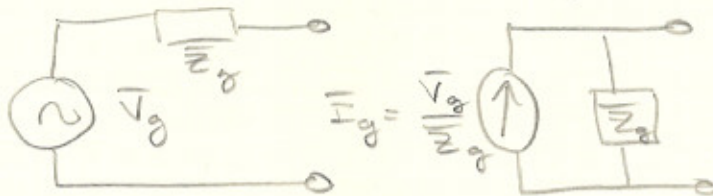


Nodal Equations

consider the following system.

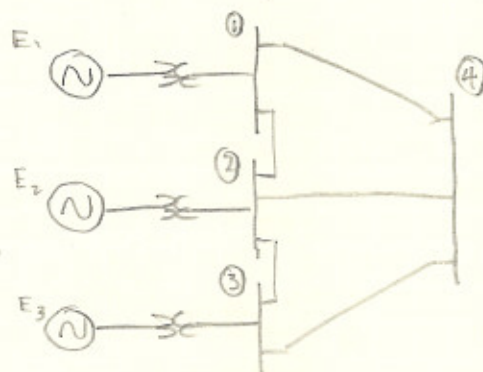

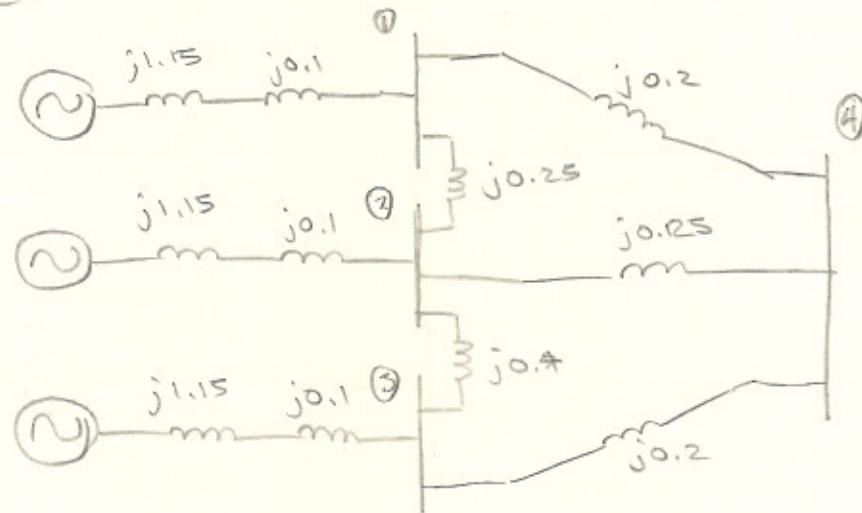Let the PU impedance diagram for the above have:



we may easily write the nodal equation by first converting voltage sources to current sources as follows.