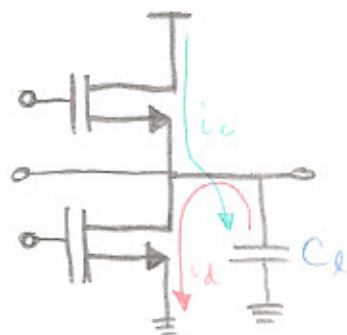


ENHANCED LOAD


$$dV_c = \frac{1}{C_L} i_c(t) dt$$

$$\int_{V_{out}^0}^{V_{out}^1} dV_c = \frac{1}{C_L} \int_0^{\Delta t_{0 \rightarrow 1}} i_c(t) dt$$


assume $i_c(t) = I_c = \text{constant}$.

$$\therefore V_{out}^1 - V_{out}^0 = \frac{I_c}{C_L} (\Delta t_{0 \rightarrow 1})$$

$$\Delta t_{0 \rightarrow 1} = \frac{(V_{out}^1 - V_{out}^0) C_L}{I_c}$$

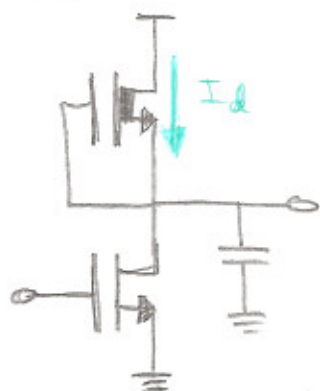DEPLETION LOAD

$$\Delta t_{0 \rightarrow 1} = \frac{(V_{out}^1 - V_{out}^0) C_L}{I_d}$$

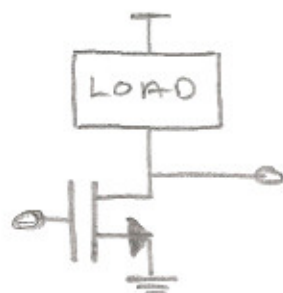
DERIVATION

$$V_{out} = I_d \cdot R_{ch}$$

$$R_{ch} = R_{no} \cdot \frac{l}{w}$$

$$R_{no} = f(I_d)$$

$$\left(\frac{l}{w} \right)_e = \frac{1}{R_{no}} \cdot \frac{V_{out}^0}{I_d}$$

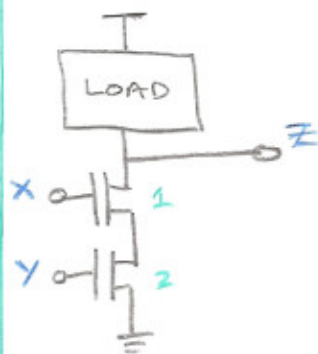
NAND

$$Z = \overline{X \cdot Y}$$

$$R_{ch_z} = R_{ch_1} + R_{ch_2}$$

$$R_{no} \left(\frac{l}{w} \right)_e = R_{no} \left(\frac{l}{w} \right)_1 + R_{no} \left(\frac{l}{w} \right)_2$$


$$\left(\frac{l}{w} \right)_i = \frac{1}{n} \left(\frac{l}{w} \right)_e \quad \text{if} \quad \left(\frac{l}{w} \right)_1 = \left(\frac{l}{w} \right)_2$$

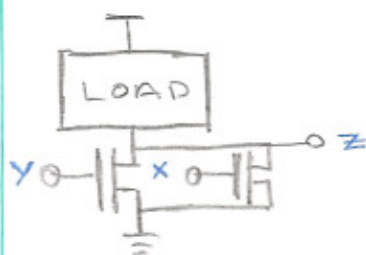NOR

$$Z = \overline{X + Y}$$

COMPLEX N-MOS

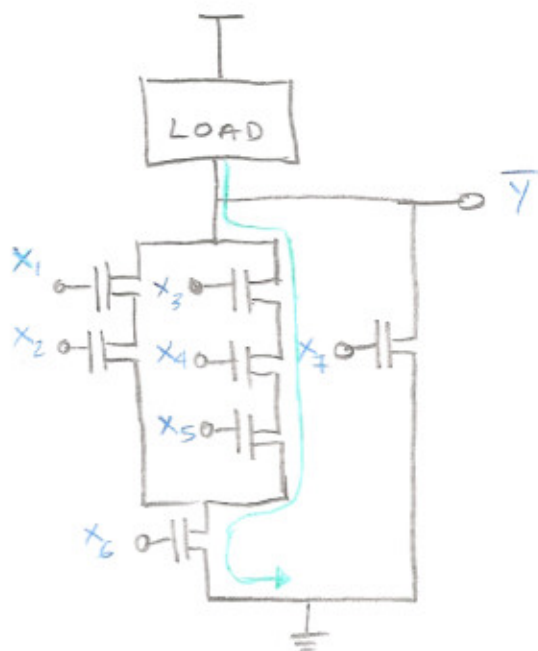EX: $Y = (X_1 \cdot X_2 + X_3 \cdot X_4 \cdot X_5) \cdot X_6 + X_7$



$$\left(\frac{l}{w} \right)_i = \frac{1}{m} \left(\frac{l}{w} \right)_e$$

m in our case is 4.