

$$Y_{bus} = \begin{bmatrix} 2 & -1 & 0 \\ -1 & 2.25 & -1 \\ 0 & -1 & 2.18 \end{bmatrix} \Omega^{-1}$$

inverting Y_{bus}

$$Z_{bus} = \begin{bmatrix} 0.6935 & 0.3871 & 0.1774 \\ 0.3871 & 0.7742 & 0.3548 \\ 0.1774 & 0.3548 & 0.6209 \end{bmatrix}$$

this is what we are interested in.
 $\rightarrow Z_{33}$

$$V_{3g} = V_{30} = 11V$$

$$I_f = \frac{-11}{0.6209} = -17.72A$$

$$V_{1f} = -17.72 \cdot 0.1774 = -3.14V$$

$$V_{2f} = -17.72 \cdot 0.3548 = -6.28V$$

$$V_{3f} = -17.72 \cdot 0.6209 = -11V$$

$$I_{12f} = \frac{-3.14 - (-6.28)}{1} = 3.14 A$$

$$I_{28f} = \frac{-6.28 - 0}{4} = -1.57 A$$

$$I_{23f} = \frac{-6.28 - (-11)}{1} = 4.72 A$$

$$I_{G11f} = \frac{0 - (-3.14)}{1} = 3.14 A$$

$$I_{E23f} = \frac{0 - (-11)}{1} = 11 A$$

$$I_{120} = \frac{11.5 - 10}{1} = 1.5 A$$

$$\therefore I_{12} = I_{120} + I_{12f}$$

$$= 1.5 + 3.14 = 4.64 A.$$

$$V_1 = V_{10} + V_{1f} = 11.5 + (-3.14) = 8.36 V$$

$$V_2 = V_{20} + V_{2f} = 10 + (-6.28) = 3.72 V$$

$$V_3 = V_{30} + V_{3f} = 11 + (-11) = 0 V$$

Note: Once the Z_{bus} (or column of it) is found the solution for the fault voltages and current flows immediately


Note: If the fault occurs on bus #2 (to ground) then the fault at bus 2 is

$$I_f = \frac{-10}{0.7742} = -12.92A$$

Note: the prefault voltages are generally obtained from the load flow solution of the system, for this load flow solution; an admittance matrix Y_{bus} is known. This matrix however omits generator and load branch impedances. To form the Y_{bus} , all is necessary is to add generator and load admittances to the diagonal elements of Y_{bus}

$$Y_{bus} = Y_{bus} + \begin{bmatrix} \text{diagonal} \\ \text{source and} \\ \text{Load} \\ \text{admittances} \end{bmatrix}$$

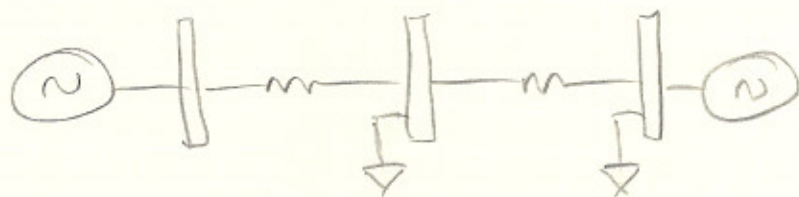EX: Building up your Y_{bus} for the previous example.




$$Y_{bus} = \begin{bmatrix} 1 & -1 & 0 \\ -1 & 2 & -1 \\ 0 & -1 & 1 \end{bmatrix}$$

Including source and load admittances, then

$$\underline{Y}_{bus} = \begin{bmatrix} 1 & -1 & 0 \\ -1 & 2 & -1 \\ 0 & -1 & 1 \end{bmatrix} + \begin{bmatrix} 1 & 0 & 0 \\ 0 & 0.25 & 0 \\ 0 & 0 & 1.18 \end{bmatrix}$$

BUILDING ZBUS

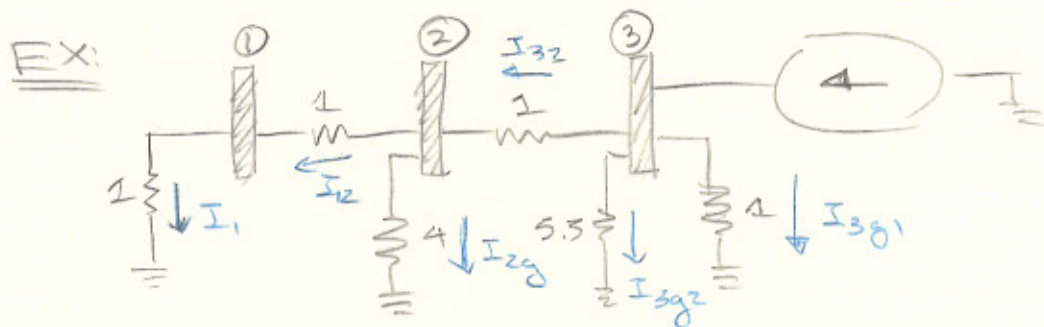The terms of Z_{bus} can also be found directly by injecting a current into each bus in turn finding the corresponding bus voltages



let $I_1 = 1$ could be any value.

$$V_1 = 1$$

$$I_{12} = 1$$

$$V_2 = 2V$$

$$I_{2g} = 0.5A$$

$$I_{32} = 1.5A$$

$$V_3 = 2 + 1.5 = 3.5V$$

$$I_{3g2} = 0.64A$$

$$I_{3g1} = 3.5A$$


$$I_3 = 5.64A$$

$$\therefore \frac{V_1}{I_3} = Z_{13} = 0.1774$$

$$\frac{V_2}{I_3} = Z_{23} = 0.3548$$

$$i. \quad \frac{V_3}{S_3} = Z_{33} = 0.6210$$

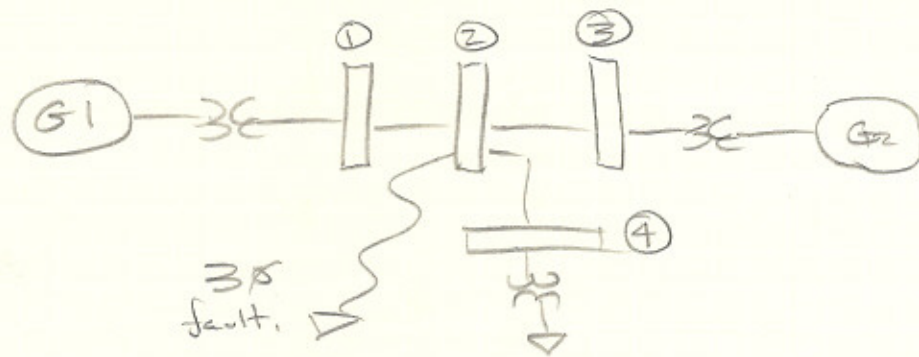EX: Given the following, determine the system voltages and currents for a 3 ϕ fault on bus #2, solve directly without the use of Zbus method.



$$Z_{12} = Z_{23} = Z_{24} = j0.1 \text{ pu}$$

$$Z_{G1} = Z_{G2} = j0.3 \text{ pu}$$

$$Z_{T1} = Z_{T2} = Z_{T3} = j0.1 \text{ pu}$$

Prefault load flow solution gave

| | V | S |
|---|----------------|---------------|
| 1 | $1.06 + j0.12$ | $0.4 + j0.26$ |
| 2 | $1.04 + j0.08$ | $0 + 0j$ |
| 3 | $1.06 + j0.12$ | $0.4 + j0.26$ |
| 4 | $1 + 0j$ | $-0.8 - j0.4$ |