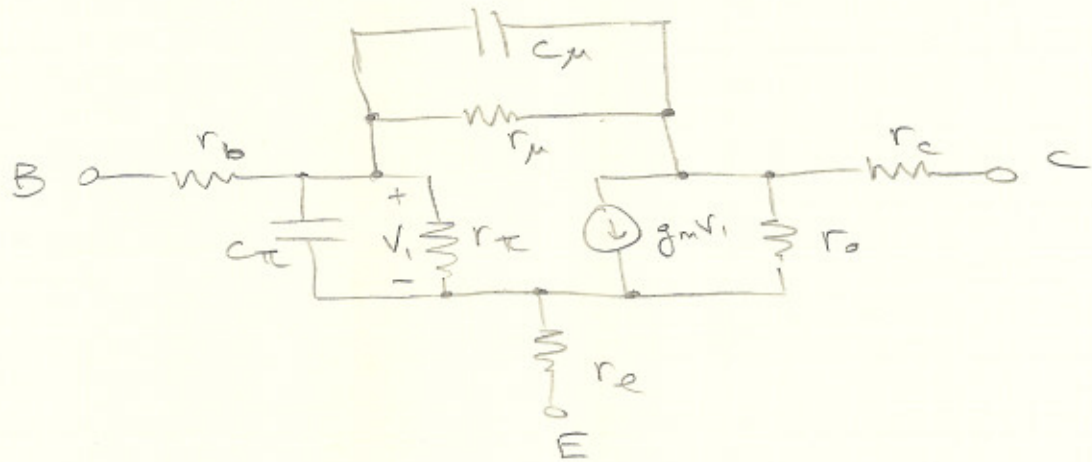


Complete Bipolar transistor model

Continuing to common base....

$R_i //$


$R_L \rightarrow \infty$ $R_i \approx r_{\pi} // R_E$ } max i/p resistance

$$r_e = \frac{\alpha}{g_m} \quad (10 \Omega)$$

$$r_{\pi} = \frac{\beta}{g_m} \quad (1 k\Omega)$$

normally, common base is R_i is close to r_e

$R_o //$

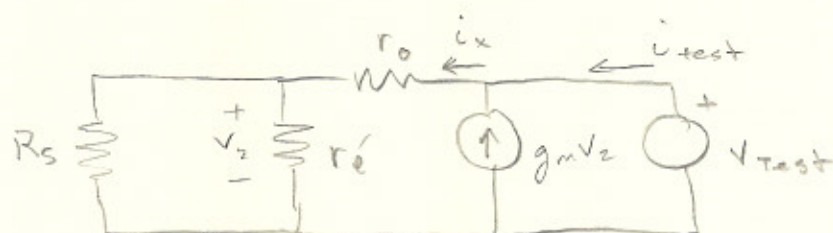

$$R_o = \frac{V_{test}}{i_{test}}$$

$$i_x = \frac{V_{test}}{r_o + R_s \parallel r_e'}$$

$$V_z = \frac{R_s \parallel r_e'}{r_o + R_s \parallel r_e'} V_{test}$$

$$i_{test} = i_x - g_m V_z$$

$$= \frac{V_{test}}{r_o + R_s \parallel r_e'} - g_m \frac{R_s \parallel r_e'}{r_o + R_s \parallel r_e'} V_{test}$$

$$= \frac{V_{test}}{r_o + R_s \parallel r_e'} \left[1 - g_m R_s \parallel r_e' \right]$$

$$R_o = \frac{r_o + (R_s \parallel r_e')}{1 - g_m (R_s \parallel r_e')}$$


QED

note Common base is used for high o/p impedance.

SUMMARY

	a_v	a_i	R_i	R_o
CE	high $-g_m R_c$	high $\approx \beta$	med $\sim r_{\pi}$	High r_o
CC	≈ 1	high $\approx \beta$	High $r_{\pi} + (\beta+1) R_E$	low $\sim r_e + \frac{R_s}{\beta+1}$
CB	High $g_m R_c$	~ 1	low r_e	V. High $K r_o$

Current Mirror

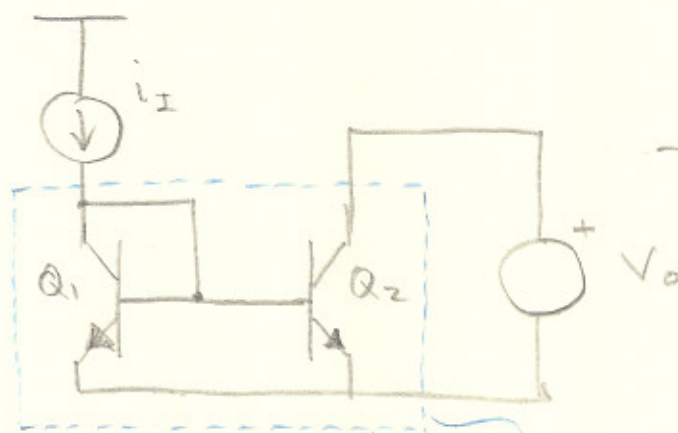

$$V_O > V_{CE\text{SAT}}$$

- to keep Q_2 is active region.

current mirror connection

$$i_{C1} \approx I_S e^{\frac{V_{BE}}{V_T}} = i_{C2} \quad (V_{BE1} = V_{BE2})$$

$$i_I = i_{C1} + i_{B1} + i_{B2} = i_C + \frac{2i_C}{\beta}$$


$$i_O = i_C$$

$$i_O = i_I \left(\frac{1}{1 + 2/\beta} \right)$$

$$\frac{1}{1 + 2/\beta} \approx 1 \quad (\text{if } \beta \text{ is large})$$

$$i_O \approx i_I$$


Current Mirror to gain

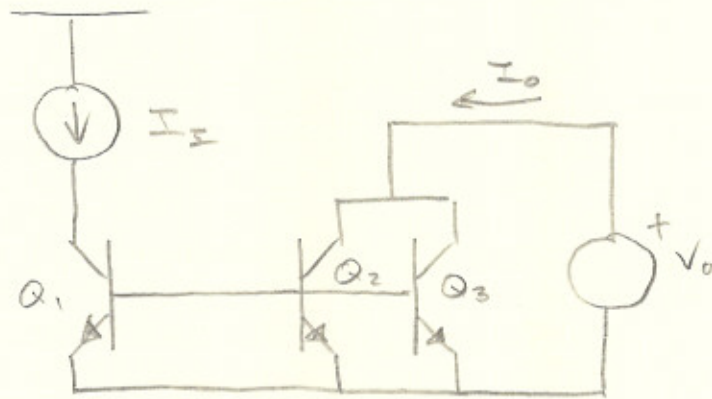

$$Q_1 = Q_2 = Q_3$$

$$I_O \approx 2 I_I$$


Current Generator

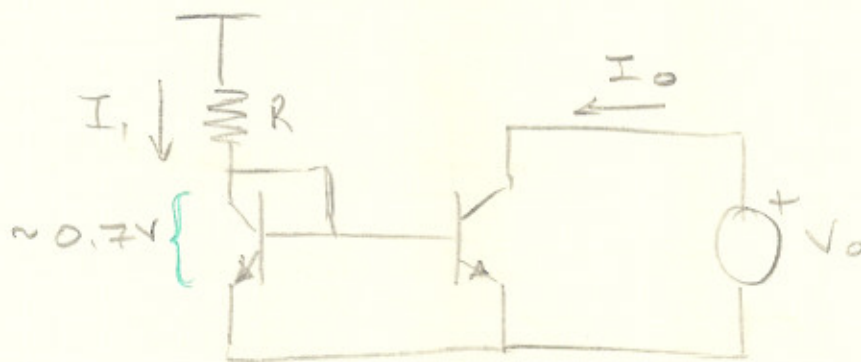

$$I_O \approx \frac{V_{BE}}{R}$$

$$I_O \approx \frac{0.7V}{R}$$

Beta Helper

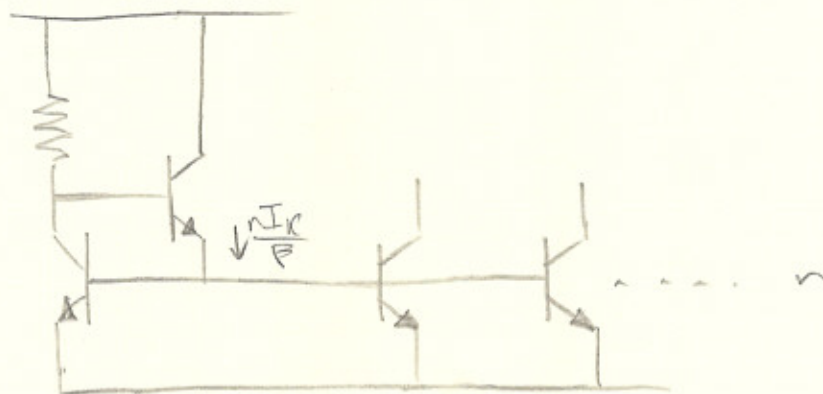

$$I_I = I_c + \frac{I_c}{\beta}$$

$$\frac{I_c}{\beta} = \frac{n I_c}{\beta^2}$$