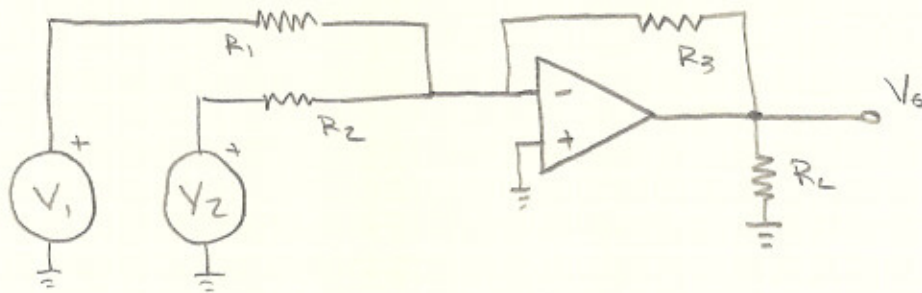


SUMMING AMPLIFIER.




$$V_o = -\frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2$$

if $R_1 = R_2 = R$

$$V_o = -\frac{R_3}{R} (V_1 + V_2)$$

DIFFERENTIAL AMPLIFIER.

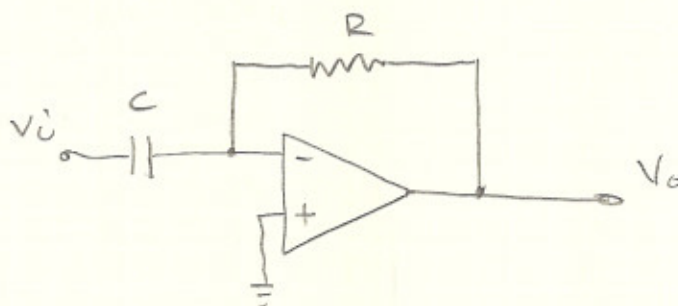


$$V_i = \frac{1}{C} \int i \, dt$$

$$i = C \frac{dV_i}{dt}$$

$$i = -\frac{V_o}{R}$$

$$\therefore V_o = -RC \frac{dV_i}{dt}$$


INTEGRATING AMP

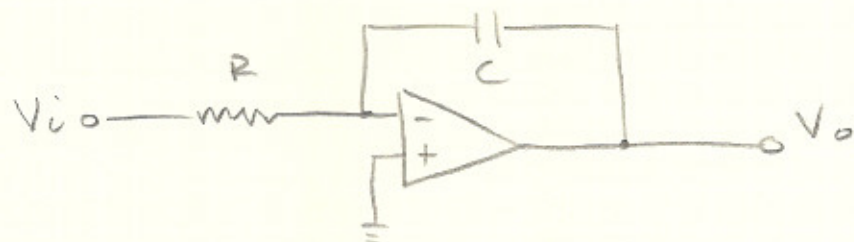

$$V_o = -\frac{1}{RC} \int V_i dt.$$

KRC FILTER

derive the expression for $T(s)$ given.

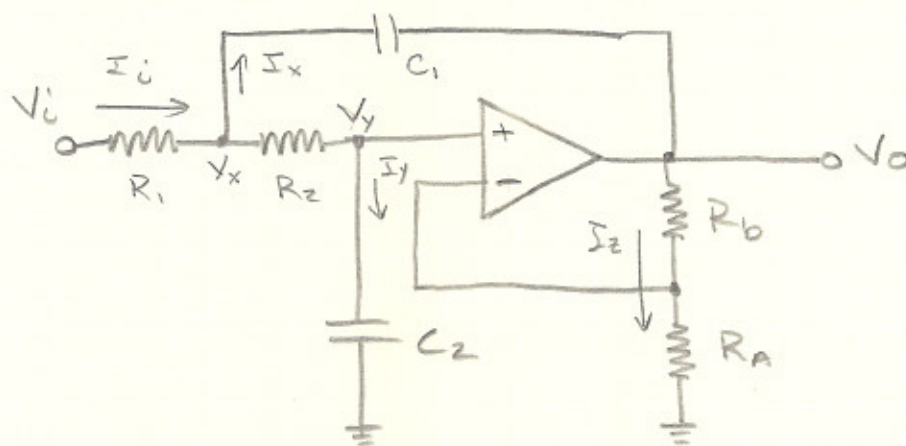

$$V_o = (R_b + R_A) I_z$$

$$R_A I_z = V^-$$

$$I_z = \frac{V^-}{R_A}$$

$$V_o = (R_b + R_A) \frac{V^-}{R_A}$$

$$V^- = \left(\frac{R_A}{R_A + R_b} \right) V_o$$

$$V^- = V^+$$

$$\therefore V^+ = \frac{V_o}{1 + \frac{R_b}{R_a}}$$

$$\text{let } k = 1 + \frac{R_b}{R_a}$$

$$\text{when } R_a = R_b \Rightarrow k = 2$$

$$R_a = 0 \Rightarrow k = \infty$$

$$R_b = 0 \Rightarrow k = 1$$

using nodal analysis, then

$$I_i = I_x + I_y \quad (1)$$

$$V_y = V^+ = \frac{V_o}{k}$$

$$I_i = \frac{V_i - V_x}{R_1} \quad (2)$$

$$I_x = (V_x - V_o) \# C_1 \quad (3)$$

$$I_y = \frac{V_x - V_y}{R_2} = \# C_2 V_y \quad (4)$$

$$V_x - V_y = \# C_2 R_2 V_y \quad \text{or}$$

$$V_x = (1 + \# C_2 R_2) V_y \quad (5)$$

but

$$V_y = \frac{V_o}{k}$$

$$\therefore V_x = (1 + \# C_2 R_2) \frac{V_o}{k}$$

$$\frac{V_i - V_x}{R_1} = (V_x - V_0) \# C_1 + \frac{V_x - \frac{V_0}{k}}{R_2}$$

$$\frac{V_i}{R_1} = \frac{V_x}{R_1} + V_x \# C_1 - V_0 \# C_1 + \frac{k V_x - V_0}{k R_2}$$

$$\frac{V_i}{R_1} = V_x \left\{ \frac{1}{R_1} + \# C_1 + \frac{1}{R_2} \right\} - \frac{V_0}{k} \left\{ \# C_1 k + \frac{1}{R_2} \right\}$$

$$\frac{V_i}{R_1} = V_x \left\{ \frac{R_1 + R_2 + \# C_1 R_1 R_2}{R_1 R_2} \right\} - \frac{V_0}{k R_2} \left\{ 1 + \# C_1 R_2 k \right\}$$

$$\frac{V_i}{R_1} = (1 + \# C_2 R_2) \frac{V_0}{k} \left\{ \frac{R_1 + R_2 + \# C_1 R_1 R_2}{R_1 R_2} \right\} - \frac{V_0}{k R_2} \left\{ 1 + \# C_1 R_2 k \right\}$$

$$\frac{V_i}{R_1} = \frac{V_0}{k} \left\{ \frac{R_1 + R_2 + \# C_1 R_1 R_2 + \# C_2 R_1 R_2 + \# C_2 R_2^2 + \#^2 C_1 C_2 R_1 R_2}{R_1 R_2} \right\} - \frac{1}{R_2} \left\{ 1 + \# C_1 R_2 k \right\}$$

$$\frac{V_0}{V_i} = \frac{k / C_1 C_2 R_1 R_2}{\#^2 + \left[\frac{(1-k) C_1 R_1 + C_2 R_1 + C_2 R_2}{C_1 C_2 R_1 R_2} \right] \# + \frac{1}{C_1 C_2 R_1 R_2}}$$

Sensitivities

$$\omega_0 = R_1^{-1/2} C_1^{-1/2} R_2^{-1/2} C_2^{-1/2}$$

$$S_{R_1}^{\omega_0} = S_{R_2}^{\omega_0} = S_{C_1}^{\omega_0} = S_{C_2}^{\omega_0} = -\frac{1}{2}$$

for Q from $S_x^y = \frac{y}{x} \frac{\partial y}{\partial x}$

$$S_{R_1}^Q = -S_{R_2}^Q = Q \sqrt{R_2 C_2 / R_1 C_1} - \frac{1}{2}$$

$$S_{C_1}^Q = -S_{C_2}^Q = Q \left[\sqrt{R_2 C_2 / R_1 C_1} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} \right] - \frac{1}{2}$$

$$S_k^Q = Q k \sqrt{R_1 C_1 / R_2 C_2}$$

$$S_{R_A}^Q = -S_{R_B}^Q = Q(1-k) \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

for equal component design, Q sensitivities simplify to

$$S_{R_1}^Q = -S_{R_2}^Q = Q - \frac{1}{2}$$

$$S_{C_1}^Q = -S_{C_2}^Q = 2Q - \frac{1}{2}$$

$$S_k^Q = 3Q - 1$$

$$S_{R_A}^Q = -S_{R_B}^Q = 1 - 2Q$$

for unity design we have:

$$S_{R_1}^Q = -S_{R_2}^Q = \frac{1 - \frac{R_1}{R_2}}{2(1 + R_1/R_2)}$$

$$S_{C_1}^Q = -S_{C_2}^Q = \frac{1}{2}$$


note: since Q sensitivities of the equal component design increase with Q , they may become unacceptable at high Q 's.

Another important quality to watch is S_k^Q , this is of concern at high Q b/c a slight mismatch in R_0/R_A ratio may drive Q to infinity, this will result in oscillating behaviour.

It should be noted that by contrast unity gain designs offer much lower sensitivities.

The designer must carefully weight a number of conflicting factors before choosing a particular filter design for a given application. These include circuit simplicity, cost, component spread, tuneability, and sensitivity.

EX: Multiple feedback BP filter.

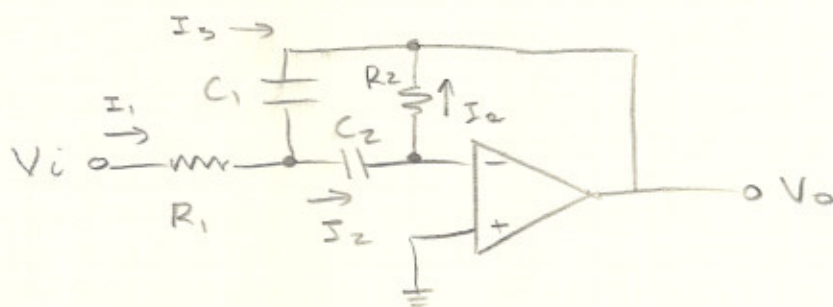

SENSITIVITY OF $T(s)$

In general:

$$S_x^{T(s)} = \frac{x}{T(s)} \frac{\partial T(s)}{\partial x}$$

let $s = j\omega$, then $T(s) = T(j\omega) = |T(j\omega)| e^{j\theta\omega}$

$$S_x^{T(j\omega)} = \frac{x}{|T(j\omega)| e^{j\theta(\omega)}} \frac{\partial}{\partial x} \{ |T(j\omega)| e^{j\theta\omega} \}$$

$$S_x^{T(j\omega)} = \frac{x}{|T(j\omega)| e^{j\theta(\omega)}} \left\{ e^{j\theta(\omega)} \frac{\partial}{\partial x} [|T(j\omega)|] + j e^{j\theta(\omega)} \frac{\partial \theta(\omega)}{\partial x} |T(j\omega)| \right\}$$

$$S_x^{|T(j\omega)|} = \text{Re } S_x^{T(j\omega)}$$

$$S_x^{\theta} = \text{Im } S_x^{T(j\omega)}$$

Ex: The transfer function of a low pass filter is given by:

$$T(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

then,

$$S_Q^{T(s)} = \frac{Q}{T} \frac{\partial T}{\partial Q} = \frac{-(\omega_0/Q)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

let $s = j\omega$

$$S_{\infty}^{|T(j\omega)|} = \operatorname{Re} S_{\infty}^{T(j\omega)} = -1$$

Ex: Band Pass filter

$$T(s) = \frac{(\omega_0/a)s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

we are asked to find

$$S_{\omega_0}^{|T(j\omega_0)|} \quad \text{and} \quad S_{\infty}^{|T(j\omega_0)|}$$


$$S_{\omega_0}^{|T(j\omega_0)|} = -2Q$$

$$S_{\infty}^{T(s)} = \frac{s^2 + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$s = j\omega_0$$

$$S_{\infty}^{T(s)} = 0$$

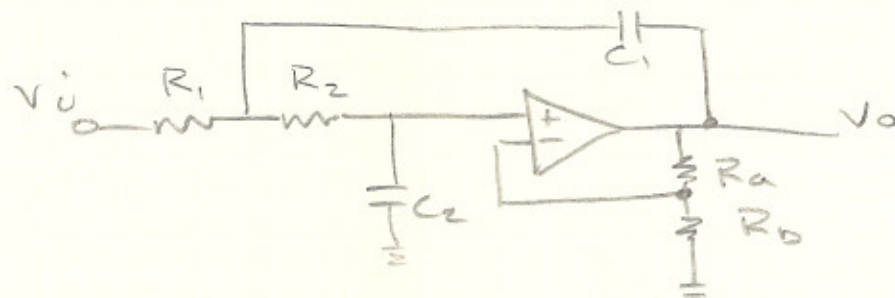Ex: Given the low pass filter shown below



$$K = 1 + \frac{R_b}{R_a}$$

$$\frac{V_o}{V_i} = T(s) = \frac{k}{R_1 C_1 C_2 R_2 s^2 + \{ (1-k) R_1 C_1 + R_1 C_2 + R_2 C_2 \} s + 1}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$Q = \frac{1}{(1-k) \sqrt{R_1 C_1 / R_2 C_2} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}}}$$

Equal component design gives.

$$R_1 = R_2 = R, C_1 = C_2 = C$$

$$\omega_0 = \frac{1}{RC} ; Q = \frac{1}{3-k}$$

Design equations are:

$$RC = \frac{1}{\omega_0}, k = 3 - \frac{1}{Q}$$

$$R_b = (k-1)R_a$$

Question: using equal components, specify elements for a 2nd order LP filter with

$$f_0 = 1 \text{ kHz}, Q = 5$$

Solution: start by choosing standard easily available capacitor, $C = 10 \text{ nF}$

$$R = \frac{1}{\omega_0 C} = \frac{1}{2\pi \times 10^3 \times 10^{-9}} = 15.92 \text{ k}\Omega$$

(use $R = 15.8 \text{ k}\Omega$, 1%)

$$K = 3 - \frac{1}{Q} = 3 - \frac{1}{5} = 2.8$$

$$\frac{R_b}{R_a} = 2.8 - 1, \text{ let us choose } R_a = 10 \text{ k}\Omega, \\ 1\% \text{ (available)}$$

$$\therefore R_b = 17.8 \text{ k}\Omega, 1\%$$

now let us investigate the effect of a 1% variation of each component in our LP design.

From previous work, we found that:

$$S_{R_1}^{w_0} = S_{C_1}^{w_0} = S_{R_2}^{w_0} = S_{C_2}^{w_0} = -\frac{1}{2}$$

hence, a 1% increase in any R_1, R_2, C_1, C_2 causes a 0.5% decrease in w_0 .

$$S_{R_1}^Q = -S_{R_2}^Q = Q - \frac{1}{2}$$

$$S_{C_1}^Q = -S_{C_2}^Q = 2Q - \frac{1}{2}$$

$$S_K^Q = 3Q - 1$$

$$S_{R_A}^Q = -S_{R_B}^Q = 1 - 2Q$$

a 1% i/c in R_1 increases Q by 4.5%. Similarly a 1% capacitive variation results in Q variation by 9.5%.

$$m = k + \sqrt{k^2 + 1}$$

$$k = \frac{n}{2Q^2} - 1$$

using unity gain option, design of a LP filter
 $f_0 = 10 \text{ kHz}$ $Q = 2$

DESIGN

Pick $C_1 = 1 \text{ nF}$

$$4Q^2 = (4)(2)^2 = 16$$

choose $n = 20$ since $n \geq 4Q^2$

then $nC = 20 \text{ nF}$

$$k = \frac{n}{2Q^2} - 1 = \frac{20}{2 \cdot 2^2} - 1 = 1.5$$

$$m = k + \sqrt{k^2 + 1} = 2.618$$

$$R = \frac{1}{\sqrt{mn} \omega_0 C}$$

$$R = \frac{1}{\sqrt{2.618 \cdot 20} \cdot 2\pi \cdot 10^4 \cdot 10^{-9}} = 2.199 \text{ k}\Omega$$

choose $2.21 \text{ k}\Omega$, 10% available

$$mR = 5.758 \text{ k}\Omega, (\text{use } 5.76 \text{ k}\Omega, 10\%)$$

Q// for the above design, investigate the effect of a 10% variation in each component.

SOL// As in the previous example, a 10% increase in any $R, C \dots$ cause a 0.5% d/c in ω_0