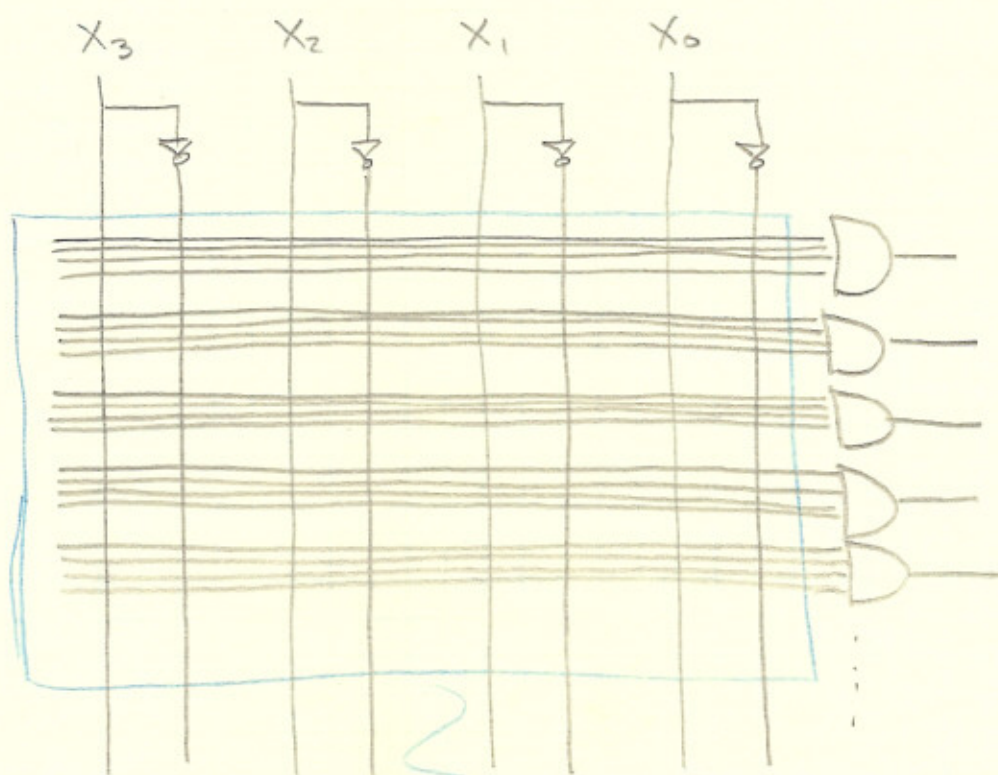


Programmable logic\* Programmable logic Array.

$$f_1 = X_3 \cdot \bar{X}_2 \cdot \bar{X}_1 \cdot X_0 + \bar{X}_3 \cdot \bar{X}_2 \cdot X_1 \cdot X_0$$


$$f_2 = X_3 \cdot \bar{X}_2 \cdot \bar{X}_1 \cdot X_0 + X_3 \cdot X_2 \cdot X_1 \cdot X_0$$

$$\begin{aligned} f_3 &= \bar{X}_3 \bar{X}_2 \bar{X}_1 \bar{X}_0 + X_3 X_2 X_1 (X_0 + \bar{X}_0) \\ &= \bar{X}_3 \bar{X}_2 \bar{X}_1 \bar{X}_0 + X_3 X_2 X_1 X_0 + X_3 X_2 X_1 \bar{X}_0 \end{aligned}$$



programmable AND field

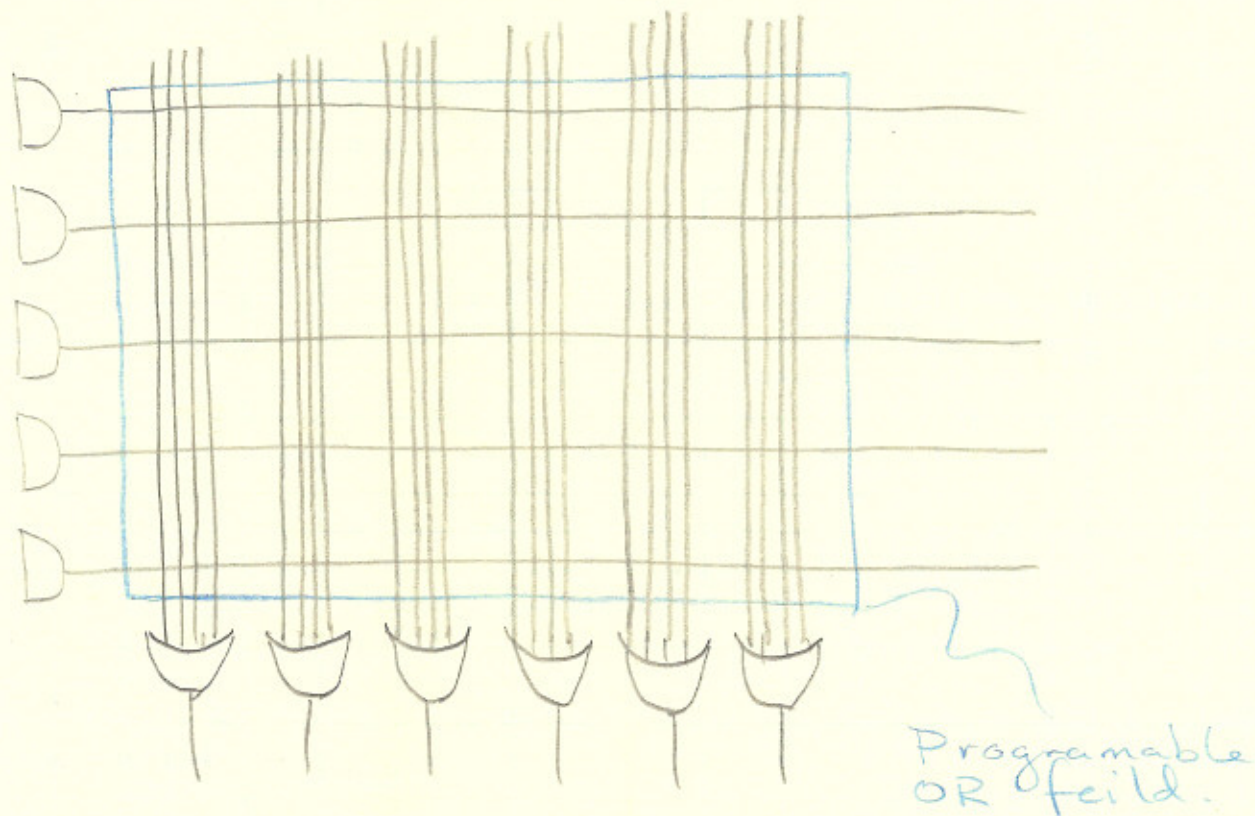Note: There must be an AND gate for every possible outcome; for 4 in i/p's there should be 16 out puts.




Note: The number of OR gates depends on the capability of the system.

By making connections at appropriate places in the two fields. The desired output circuit can be created.
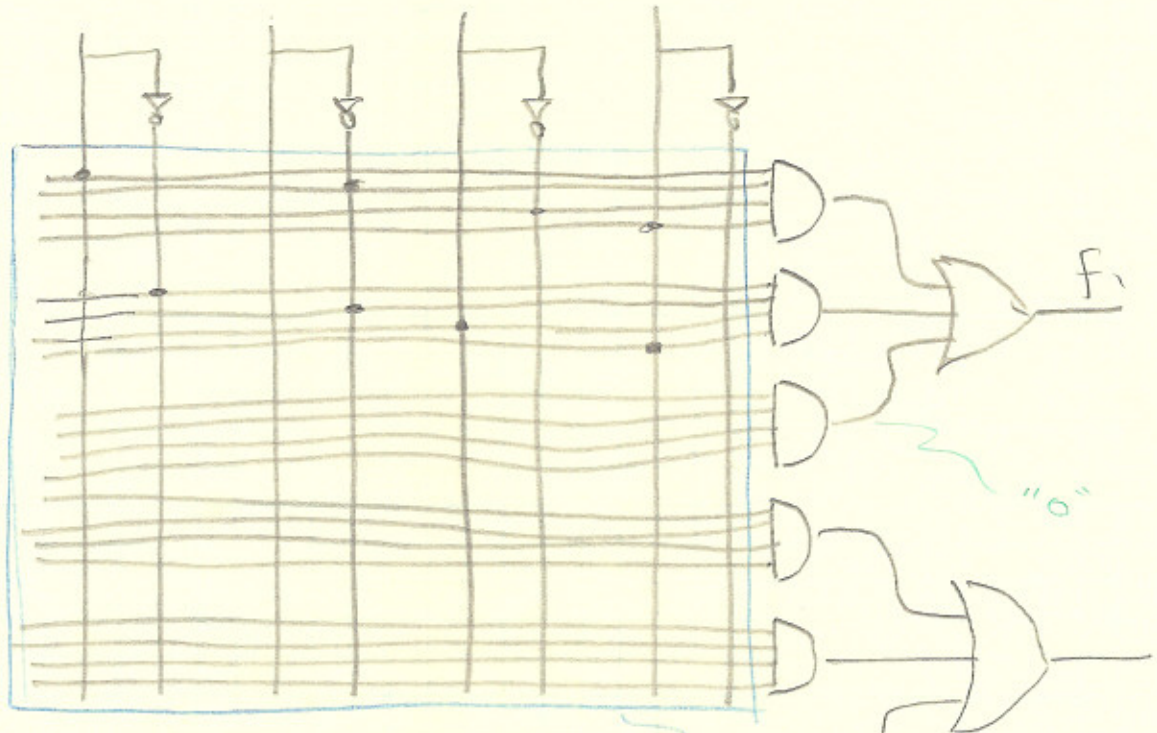
### \* Programmable Array Logic (PAL)

$$\left. \begin{array}{l} f_1 = \\ f_2 = \\ \vdots \\ f_n = \end{array} \right\} \text{same as last example}$$





Programmable ~~logic~~  
AND field

Note There are some serious disadvantages over the last device; we may end up with many more AND gates to perform the same task. The main advantage is that there is only one field to program.