


$$Y = X_2 \cdot \bar{X}_1 \cdot X_0 + \bar{X}_2 \cdot X_1 \cdot \bar{X}_0 + X_1 \cdot X_0 (X_2 + \bar{X}_2)$$

as not to
make mistakes.


| X_2 | X_1 | X_0 | Y |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Using 2-to-1 multiplexers

| S_0 | f |
|-------|-------|
| 0 | w_0 |
| 1 | w_1 |

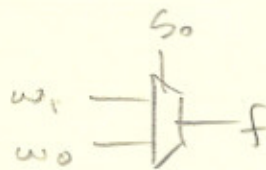

* must draw this
for full marks.

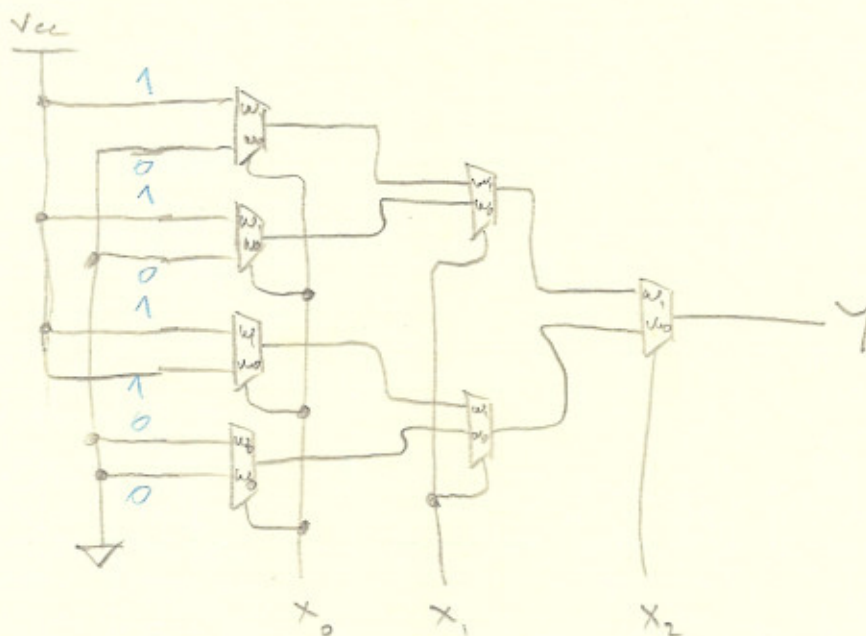

Note:




no electrical connection




electrical connection.

Demultiplexer

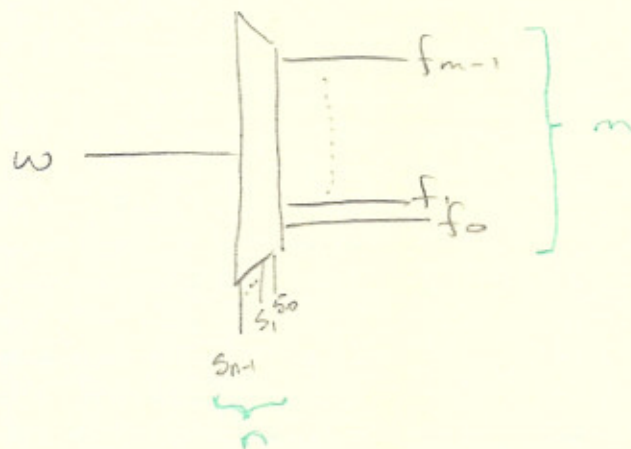


$$\underline{m = 2^n}$$

1-to-2 multiplexer

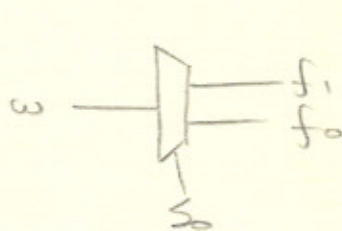


s_0 f_1 f_0
 0 1 0
 1 0 1


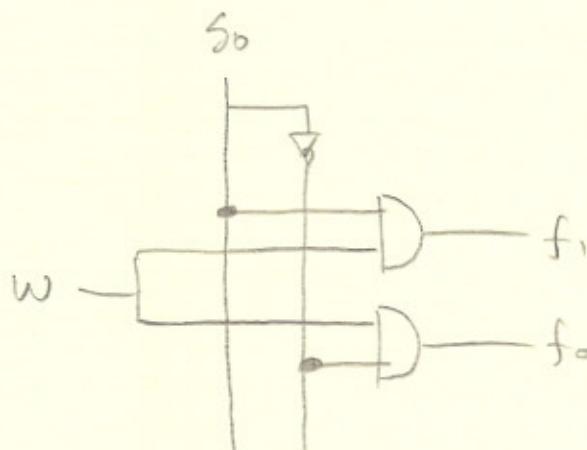


instead of
zero b/c of the
organization of
the AND gate.

4-to-1 multiplexer

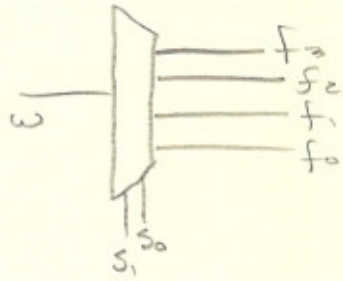


| s_0 | s_1 | f_0 | f_1 | f_2 | f_3 |
|-------|-------|-----------|-----------|-----------|-----------|
| 0 | 0 | w | \bar{w} | \bar{w} | \bar{w} |
| 1 | 0 | \bar{w} | w | \bar{w} | \bar{w} |
| 0 | 1 | \bar{w} | \bar{w} | w | \bar{w} |
| 1 | 1 | \bar{w} | \bar{w} | \bar{w} | w |

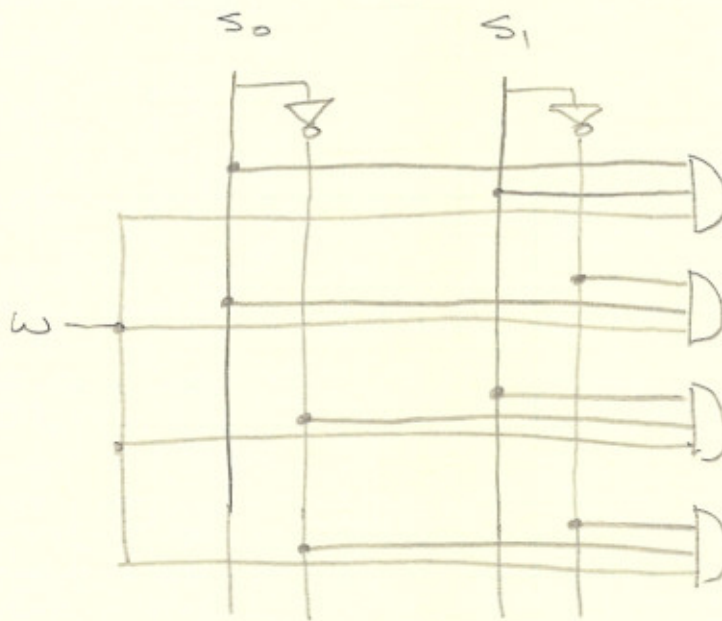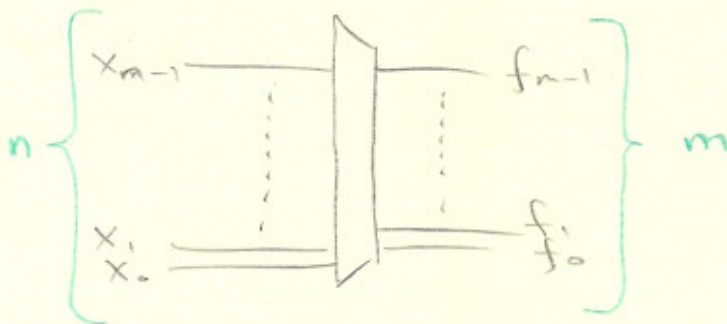
Decoder

$$\underline{\underline{m \leq 2^n}}$$


| | | | | | | | |
|-----------|-----|-------|-------|-----------|-----|-------|-------|
| x_{n-1} | ... | x_1 | x_0 | f_{m-1} | ... | f_1 | f_0 |
| 0 | | 0 | 0 | 0 | | 0 | 1 |
| 0 | | 0 | 1 | 0 | | 1 | 0 |
| 1 | | 1 | 1 | 1 | | 0 | 0 |

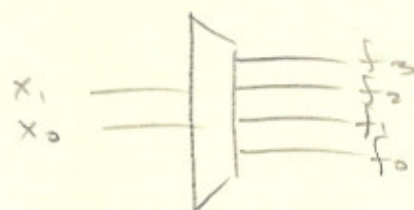Ex

| | | | | | |
|-------|-------|-------|-------|-------|-------|
| x_1 | x_0 | f_3 | f_2 | f_1 | f_0 |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |

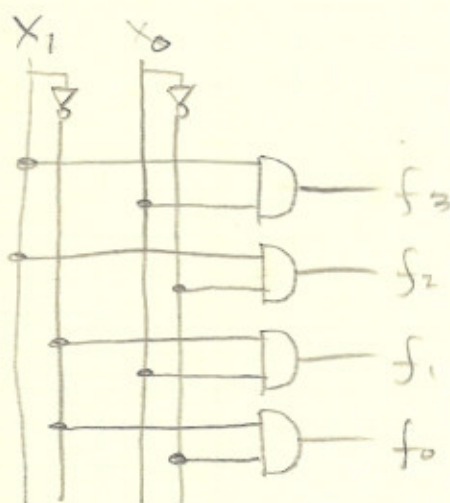


Encoder

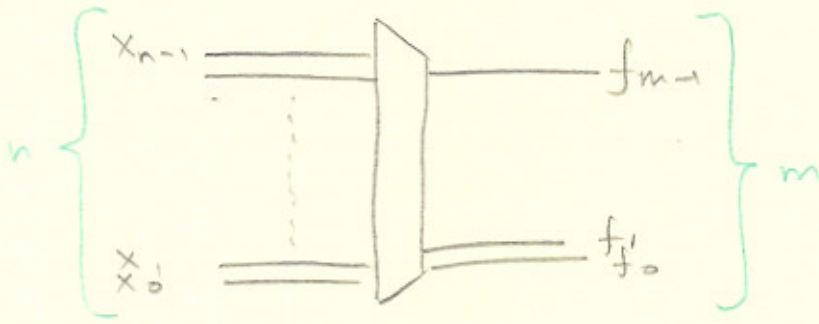

$$n \leq 2^m$$

EX

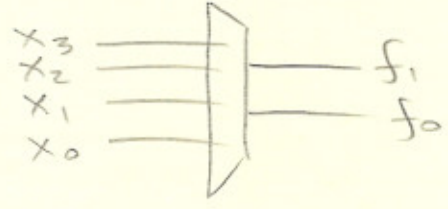

| x_3 | x_2 | x_1 | x_0 | f_1 | f_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |

