 


LOGIC CIRCUITS

- \* Truth table
- \* Minimisation by Karnaugh map.
- \* Block diagram of circuit
- \* Design of CMOS circuit
- \* Simulation.

EX:

$x_3$	$x_2$	$x_1$	$x_0$	$y_1$	$y_0$
0	0	0	0	1	0
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	1	1
1	1	1	1	1	1


	$x_3$	$\bar{x}_3$	$y_1$	
			$\bar{x}_1$	$x_1$
$x_2$	1	1	0	0
	0	1	1	1
$\bar{x}_2$	1	1	1	1
	0	1	0	1
	$\bar{x}_0$	$x_0$	$\bar{x}_0$	

	$x_3$	$y_0$	
		$x_1$	
$x_2$	1	1	0
	1	1	1
	1	1	0
	0	1	0
	$x_0$		

$$y_0 = x_3 \cdot x_0 + x_2 \cdot x_1 + x_3 \cdot x_2 + x_3 \cdot x_1$$

$$y_1 = x_3 \cdot x_0 + x_1 \cdot x_0 + \bar{x}_3 \cdot x_1 + \bar{x}_2 \cdot x_1$$
 
$$+ \bar{x}_0 \cdot x_1 \cdot \bar{x}_2 \cdot \bar{x}_3 + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0 \cdot x_3$$



For the Design of complex Cmos; refer to CCD notes. Will need to know this for test.

For the Verilog simulation, all nodes must be labeled.

```
module circuit;
  input x3, x2, x1, x0;
  output y1, y0;
  wire x3, x2, x1, x0, y1, y0, A0, A1, A2, B1, B2,
        B3, B4, C1, C2, C3, C4, C5, C6;
```

```
begin
```

```
fork
```

```
A3 = x3;
A2 = x2;
A1 = x1;
A0 = x0;
```

```
join
```

```
#2;
```

```
fork
```

```
B1 = x3 && x0;
B2 = x2 && x1;
B3 = x3 && x2;
B4 = x3 && x1;
```

```
C1 = x3 && x0;
C2 = x1 && x0;
C3 = A3 && x1;
C4 = A2 && x1;
C5 = A0 && x1 && A2 && A3;
C6 = x2 && A1 && A0 && x3;
```

```
join
```

```
#5;
```

```
fork
```

```
y0 = B1 || B2 || B3 || B4;
```

```
y1 = C1 || C2 || C3 || C4 || C5 || C6;
```



join  
#4;  
end  
end module.

note

$$C = \underbrace{!A} \&\& B$$

we can't do this because  
there is more than  
one gate involved.