
 
 
 


Half adder

a_i	b_i	C_i	S_i
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Step #1

 

Step #2

$$S_i = a_i \bar{b}_i + \bar{a}_i b_i$$

$$C_i = a_i b_i$$

 

Design of C-mos circuit
(for homework) } Step # 4

```
module half adder;
input AI, BI;
output SI, CI;
wire AI, BI, SI, CI, X1, X2, Y1, Y2;
```

```
begin
```

```
fork
```

```
X1 = !AI;
```

```
X2 = !BI;
```

```
join
```

```
#4;
```

```
fork
```

```
Y1 = AI & X2;
```

```
Y2 = BI & X1;
```

```
CI = AI & BI;
```

```
join
```

```
#4;
```

```
SI = Y1 || Y2;
```



```
#73
```

```
end
endmodule
```



Step # 5

FULL ADDER

A register

 
 


B register

  

c_{i-1}	a_i	b_i	c_i	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Step # 1

  

Step #2

$$S_i = C_{i-1} \bar{a}_i \bar{b}_i + C_{i-1} b_i a_i + \bar{C}_{i-1} \bar{a}_i b_i + \bar{C}_{i-1} a_i b_i$$
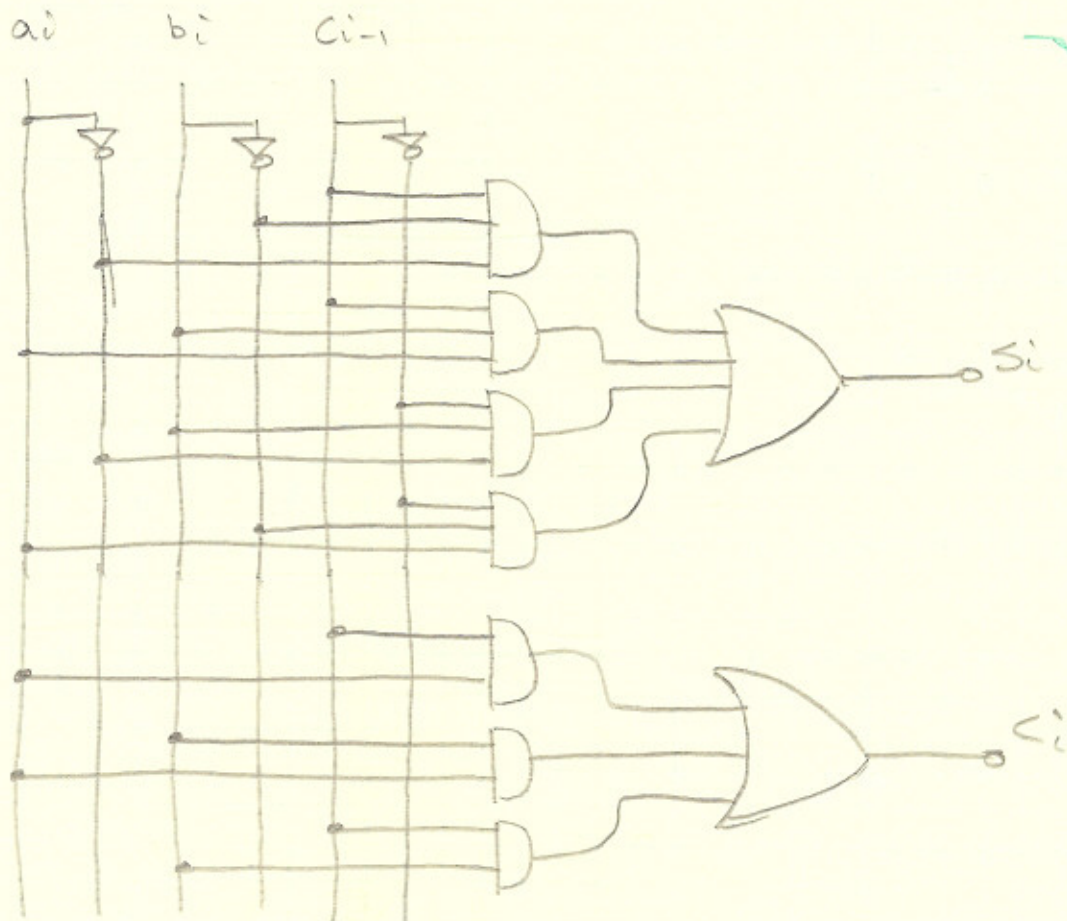
$$C_i = C_{i-1} a_i + b_i a_i + C_{i-1} b_i$$



Step #3

Design C-MOS circuit } Step #4
(homework)

```
module full_adder;
```

```
inputs AI, BI, CI1;
```

```
outputs CI, SI;
```

```
wires AI, BI, CI1, CI, SI, X1, X2, X3, Y1, Y2, Y3  
      Y4, Y5, Y6, Y7;
```

```
begin
```

```
fork
```

```
X1 = !A1;
```

```
X2 = !B1;
```

```
X3 = !CI1;
```

```
join
```

```
#4;
```

```
fork
```

```
Y1 = CI1 && X1 && X2;
```

```
Y2 = CI1 && A1 && B1;
```

```
Y3 = X3 && X1 && B1;
```

```
Y4 = X3 && A1 && X2;
```

```
Y5 = CI1 && A1;
```

```
Y6 = CI1 && B1;
```

```
Y7 = A1 && B1;
```

```
join
```

```
#4;
```

```
fork
```

```
SI = Y1 || Y2 || Y3 || Y4;
```

```
CI = Y5 || Y6 || Y7;
```

```
join
```

```
#4;
```

```
end
```

```
end module
```

Step
#5