
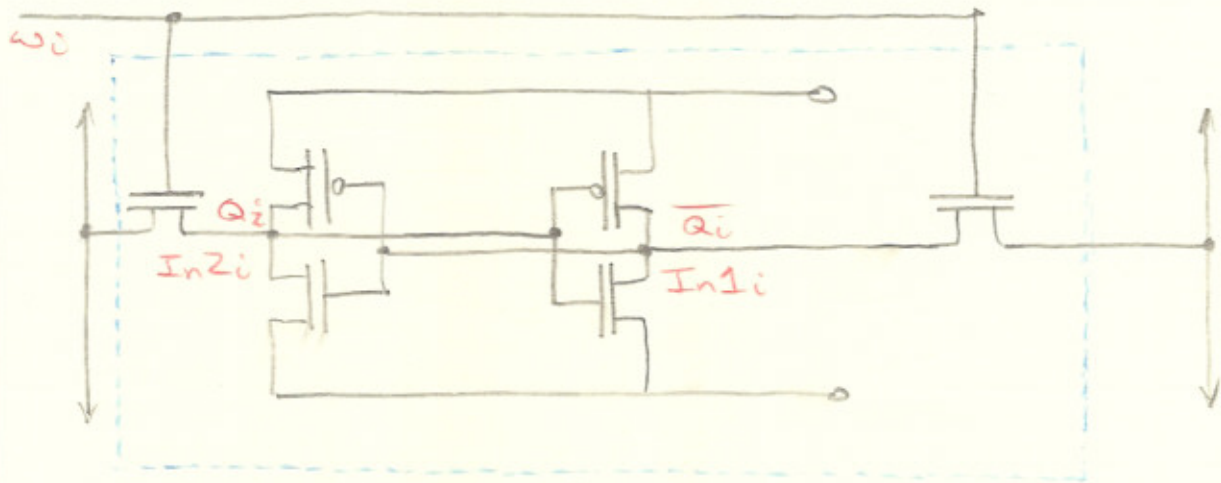



Static Ram Cell

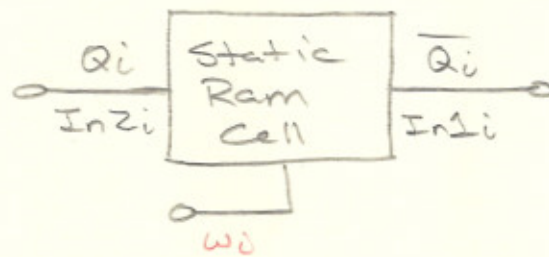


static RAM cell




Organise 4 words of 4 bits

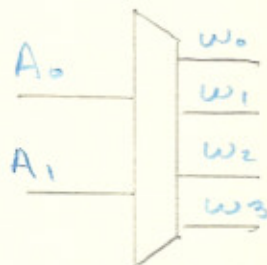

A ₀	A ₁	w ₀	w ₁	w ₂	w ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

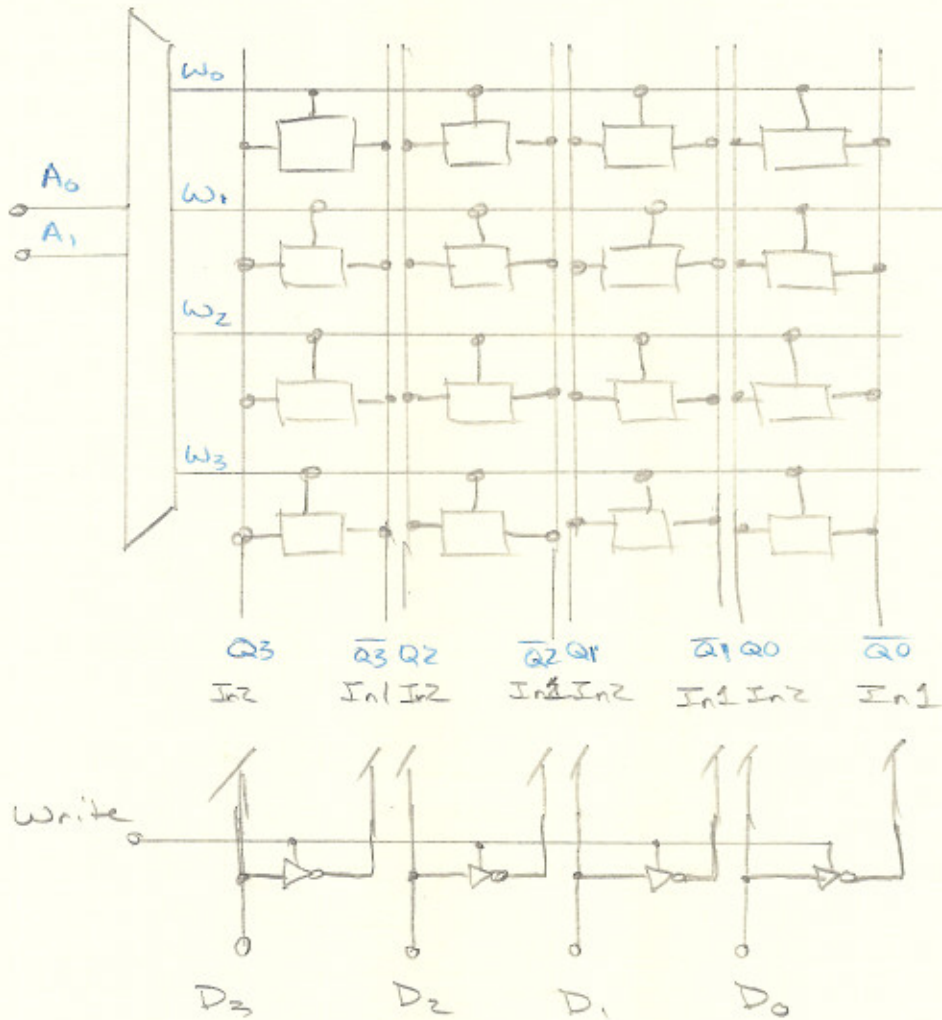

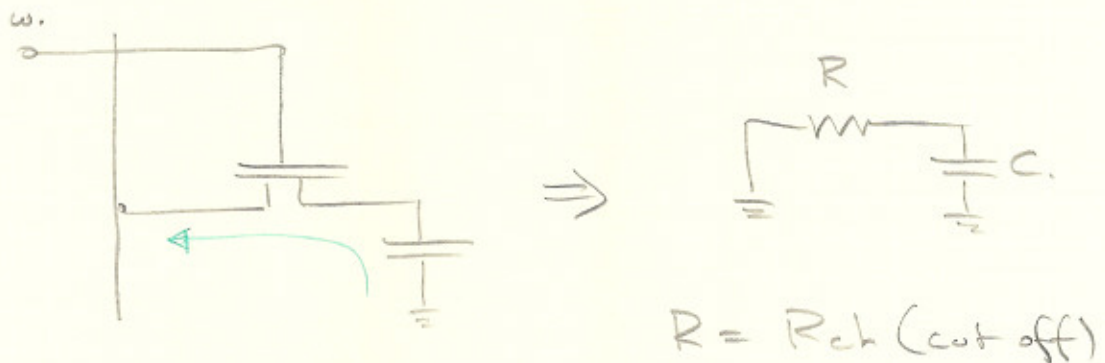We want the system to hold charge even when power is off; we investigate the cap.



$$i_c = C \frac{dv_c}{dt}$$

$$V_R + V_C = 0$$

$$R i(t) + V_C = 0$$

$$RC \frac{dv_c}{dt} + V_C = 0$$


$$RC K' + K^0 = 0$$

$$K = \frac{-1}{RC}$$

$$V_C(t) = A e^{-1/RC \cdot t} = A e^{-t/\tau}$$

$$\tau = RC$$

$$V_C(t) = V'_{\max} e^{-t/\tau}$$

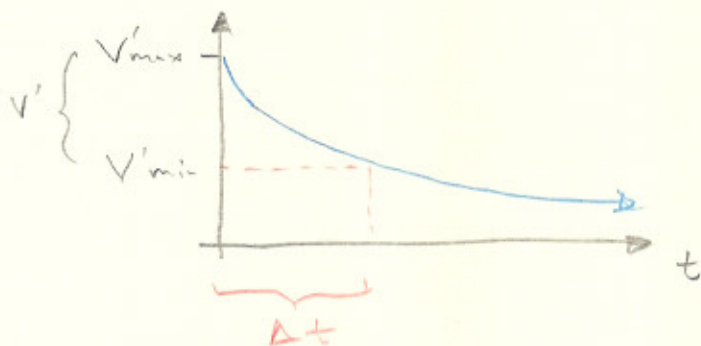

$$V_C(\Delta t) = V'_{\min}$$

$$V_C(\Delta t) = V'_{\max} e^{-\frac{\Delta t}{\tau}}$$

$$\Delta t = -\tau \ln\left(\frac{V'_{\min}}{V'_{\max}}\right)$$

We should recharge the capacitor at:

$$T_0 = \frac{\Delta t}{2}$$

\therefore @ a freq of:

$$f_0 = \frac{1}{T_0} = \frac{2}{\Delta t} = 2 \left[-2 \ln \left(\frac{V'_{min}}{V'_{max}} \right) \right]^{-1}$$

